

Joseph Nguyen


ECEN 454 Section 510

Lab date: 12 September 2024


Due date: 18 September 2024

Lab 2: Cadence Custom layout: Design Rules, Extraction, and Verification


Inverter Schematic

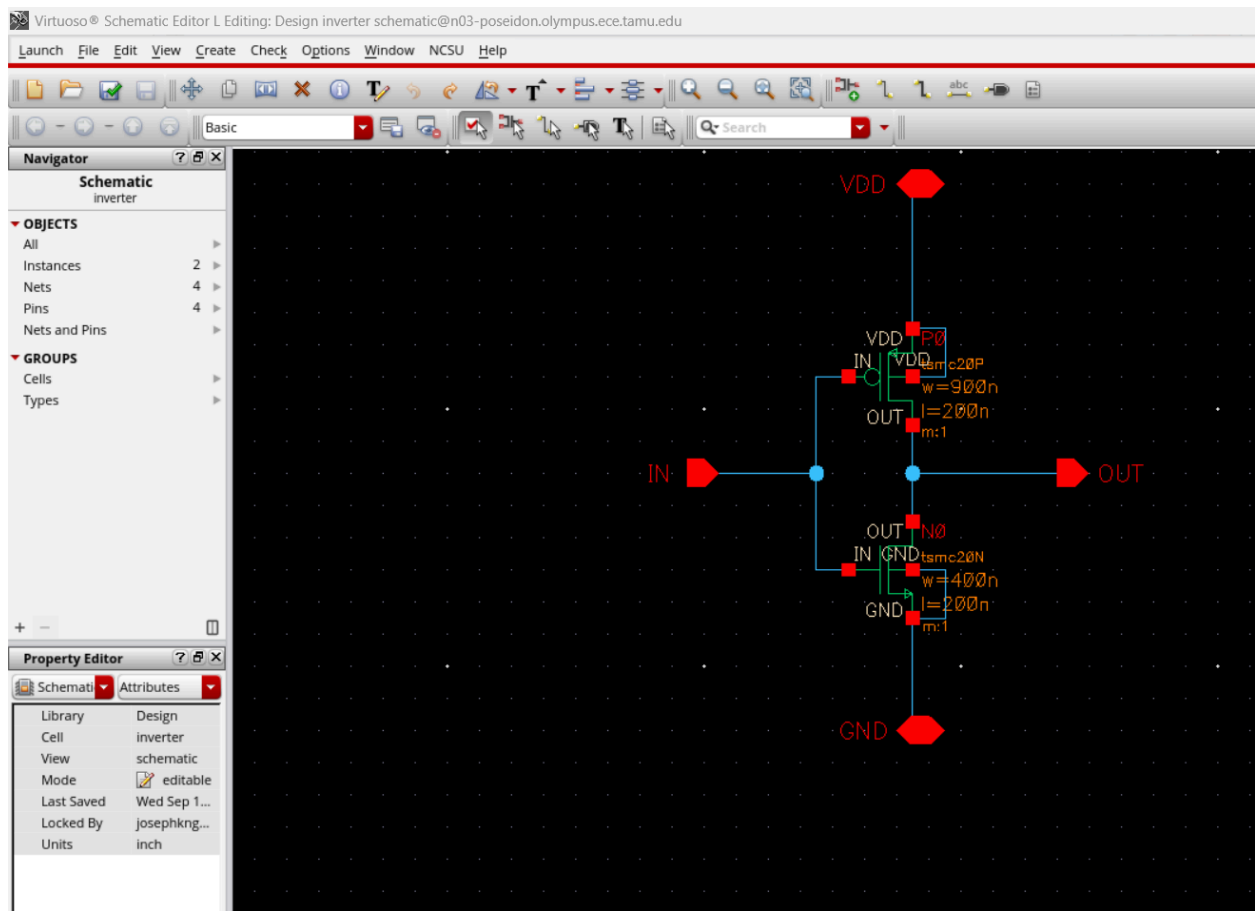

Inverter Symbol:

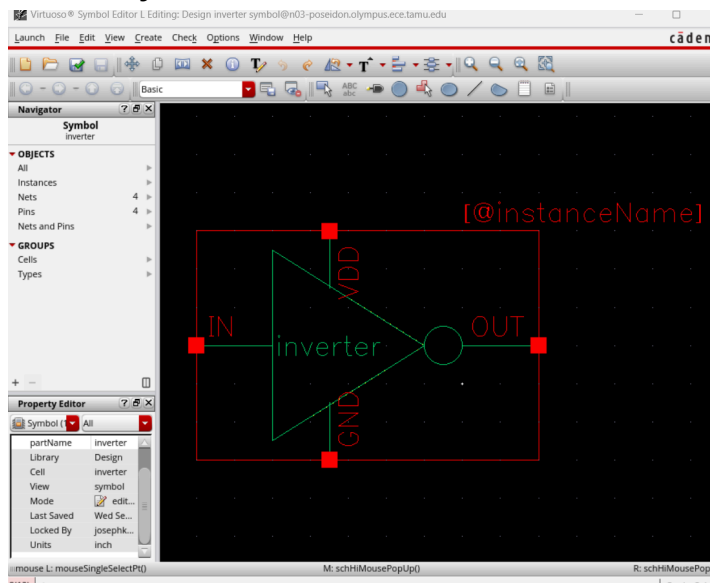

Inverter layout:

 

Inverter LVS:

Terminal correspondence points

| | | |
|----|----|-----|
| N0 | N2 | GND |
| N2 | N0 | IN |
| N1 | N1 | OUT |
| N3 | N3 | VDD |

Devices in the netlist but not in the rules:

pcapacitor

Devices in the rules but not in the netlist:


cap nfet pfet nmos4 pmos4

The net-lists match.


| | layout | schematic |
|----------------|-----------|-----------|
| | instances | |
| un-matched | 0 | 0 |
| rewired | 0 | 0 |
| size errors | 0 | 0 |
| pruned | 0 | 0 |
| active | 2 | 2 |
| total | 2 | 2 |
| | nets | |
| un-matched | 0 | 0 |
| merged | 0 | 0 |
| pruned | 0 | 0 |
| active | 4 | 4 |
| total | 4 | 4 |
| | terminals | |
| un-matched | 0 | 0 |
| matched but | | |
| different type | 0 | 0 |
| total | 4 | 4 |

Probe files from /home/ugrads/j/josephknguyen02/ecen454_714/LVS/schematic


Nand2 schematic:

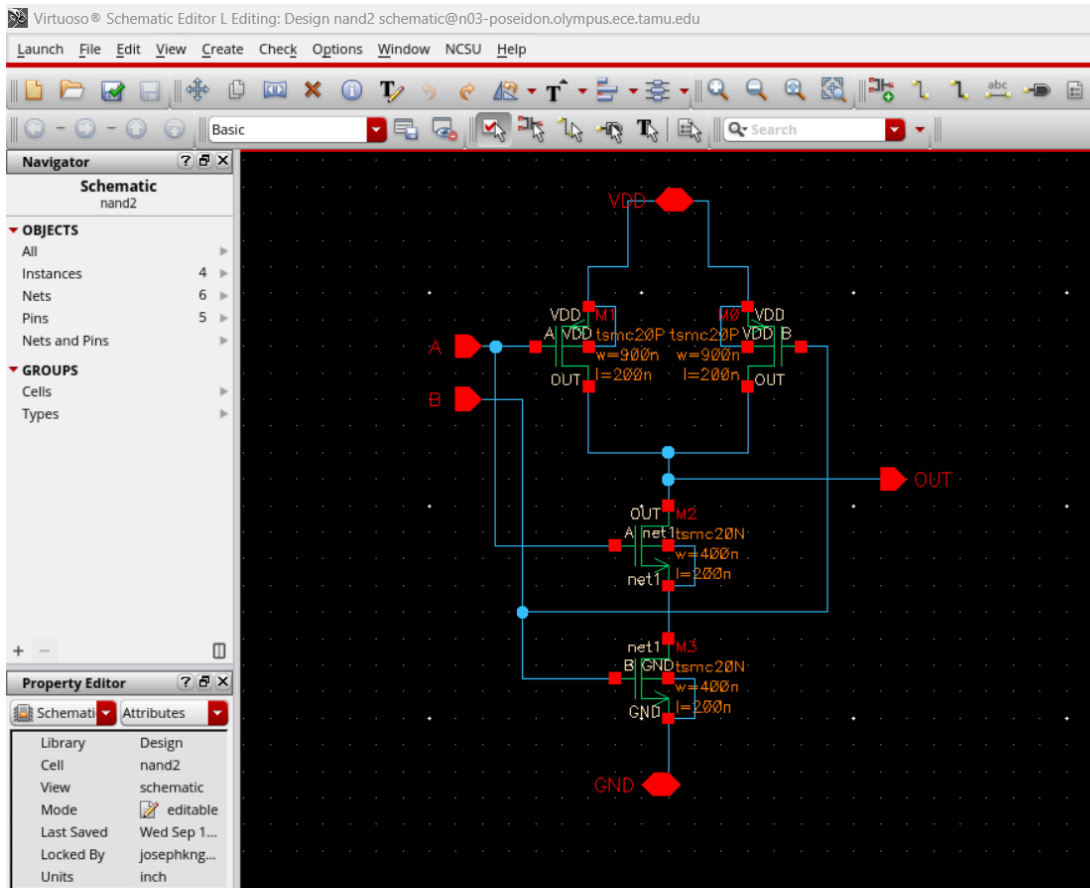

Nand2 symbol:

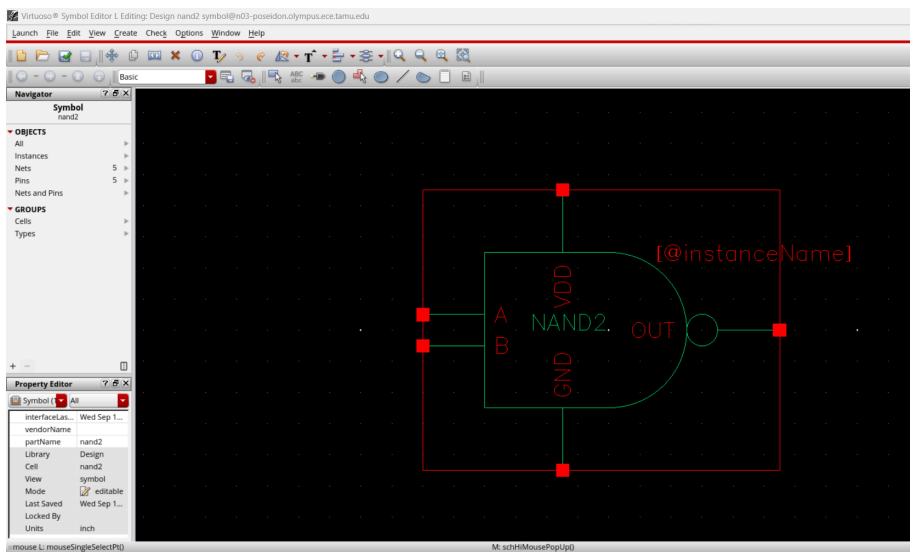

Nand2 layout:

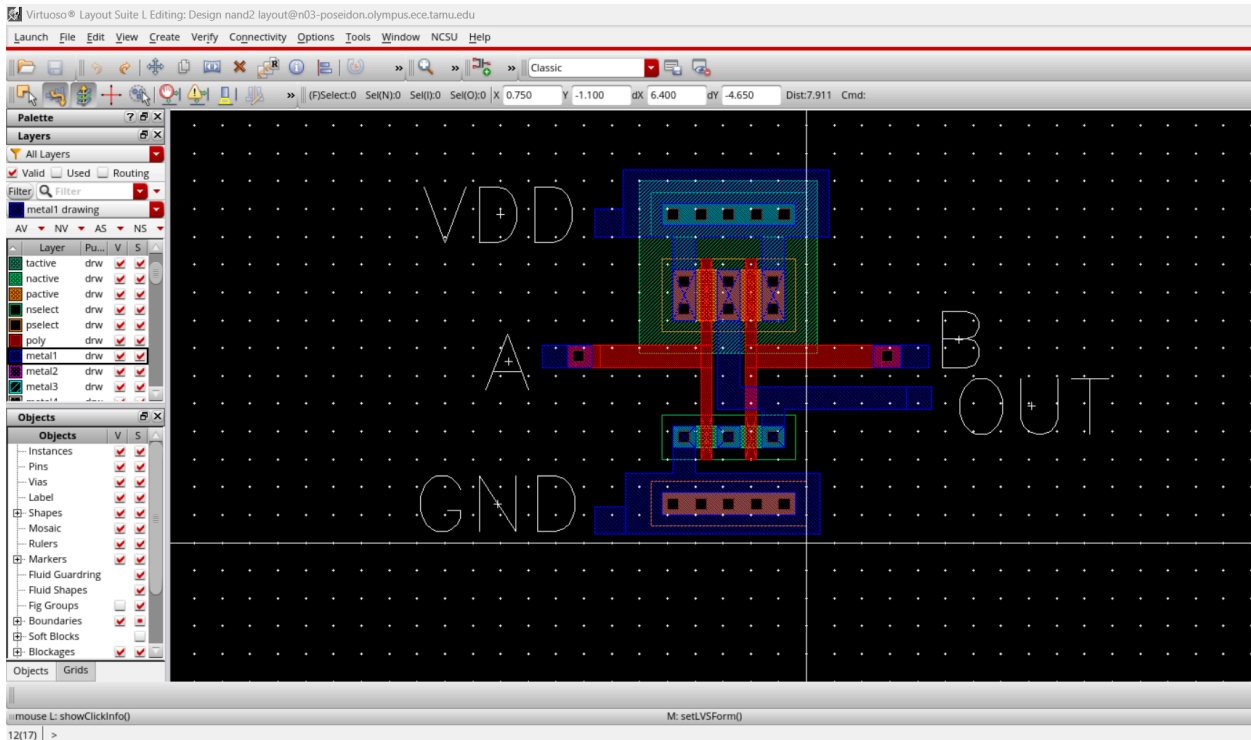

Nand2 LVS:

```
Terminal correspondence points
N0      N2      GND
N2      N0      IN
N1      N1      OUT
N3      N3      VDD

Devices in the netlist but not in the rules:
pcapacitor
Devices in the rules but not in the netlist:
cap nfet pfet nmos4 pmos4

The net-lists match.


layout schematic
instances
un-matched      0      0
rewired         0      0
size errors     0      0
pruned          0      0
active          2      2
total           2      2

nets
un-matched      0      0
merged          0      0
pruned          0      0
active          4      4
total           4      4


terminals
un-matched      0      0
matched but
different type   0      0
total           4      4

Probe files from /home/ugrads/j/josephknguyen02/ecen454_714/LVS/schematic
```


Xor2 schematic:

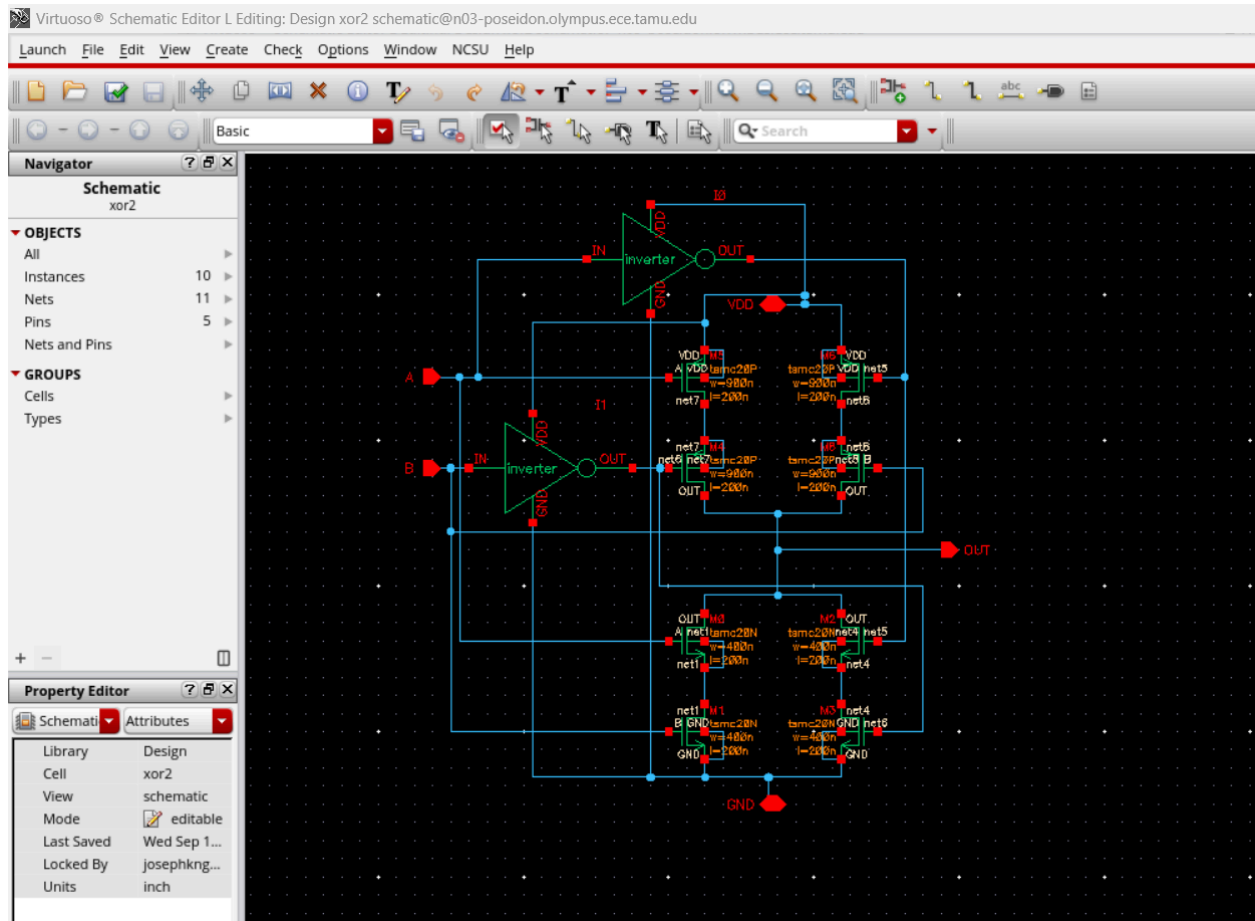

Xor2 symbol:

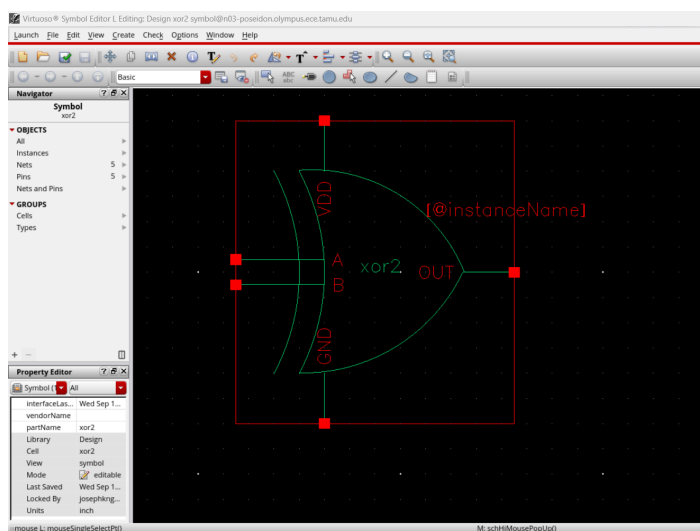

Xor2 layout:

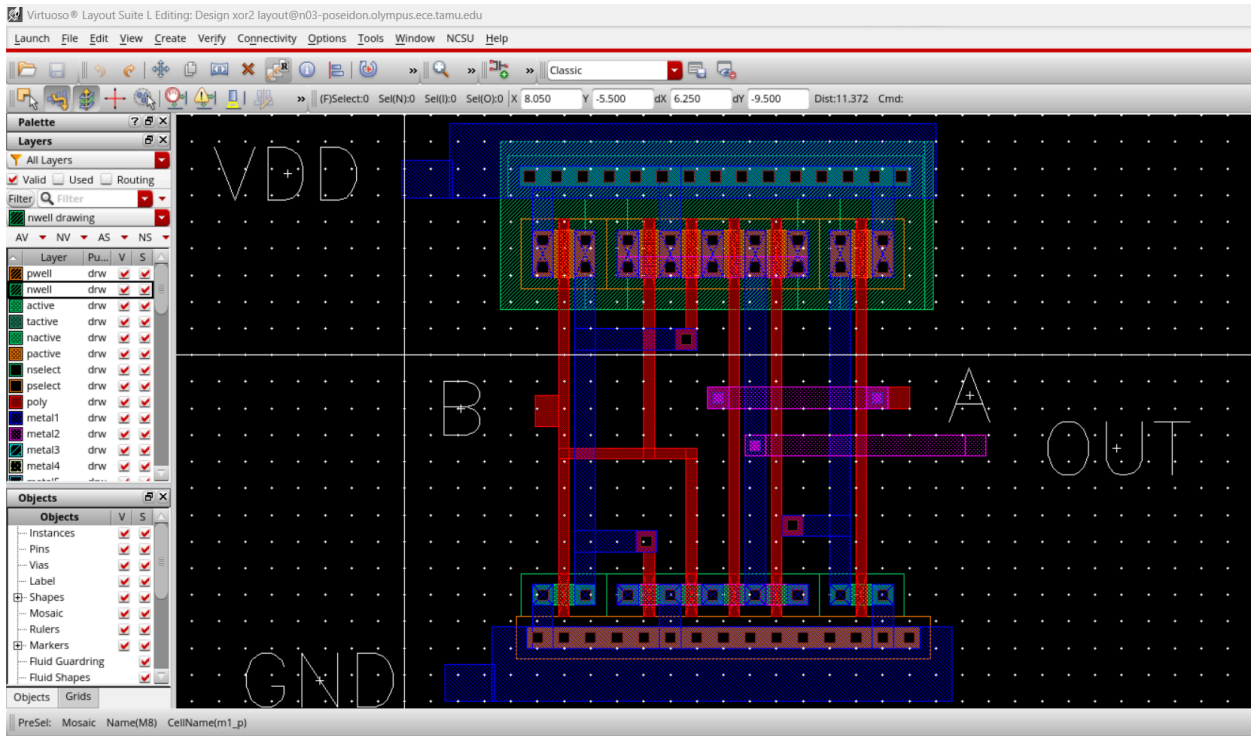

Xor2 LVS:

```
Terminal correspondence points
N0      N2      GND
N2      N0      IN
N1      N1      OUT
N3      N3      VDD

>devices in the netlist but not in the rules:
pcapacitor
>devices in the rules but not in the netlist:
cap nfet pfet nmos4 pmos4

The net-lists match.

layout schematic
instances
un-matched 0 0
rewired 0 0
size errors 0 0
pruned 0 0
active 2 2
total 2 2

nets
un-matched 0 0
merged 0 0
pruned 0 0
active 4 4
total 4 4

terminals
un-matched 0 0
matched but different type 0 0
total 4 4

>probe files from /home/ugrads/j/josephknguyen02/ecen454_714/LVS/schematic
```