

Joseph Nguyen


ECEN 454 Section 510

Lab date: 12 September 2024


Due date: 18 September 2024

Lab 2: Cadence Custom layout: Design Rules, Extraction, and Verification


Inverter Schematic

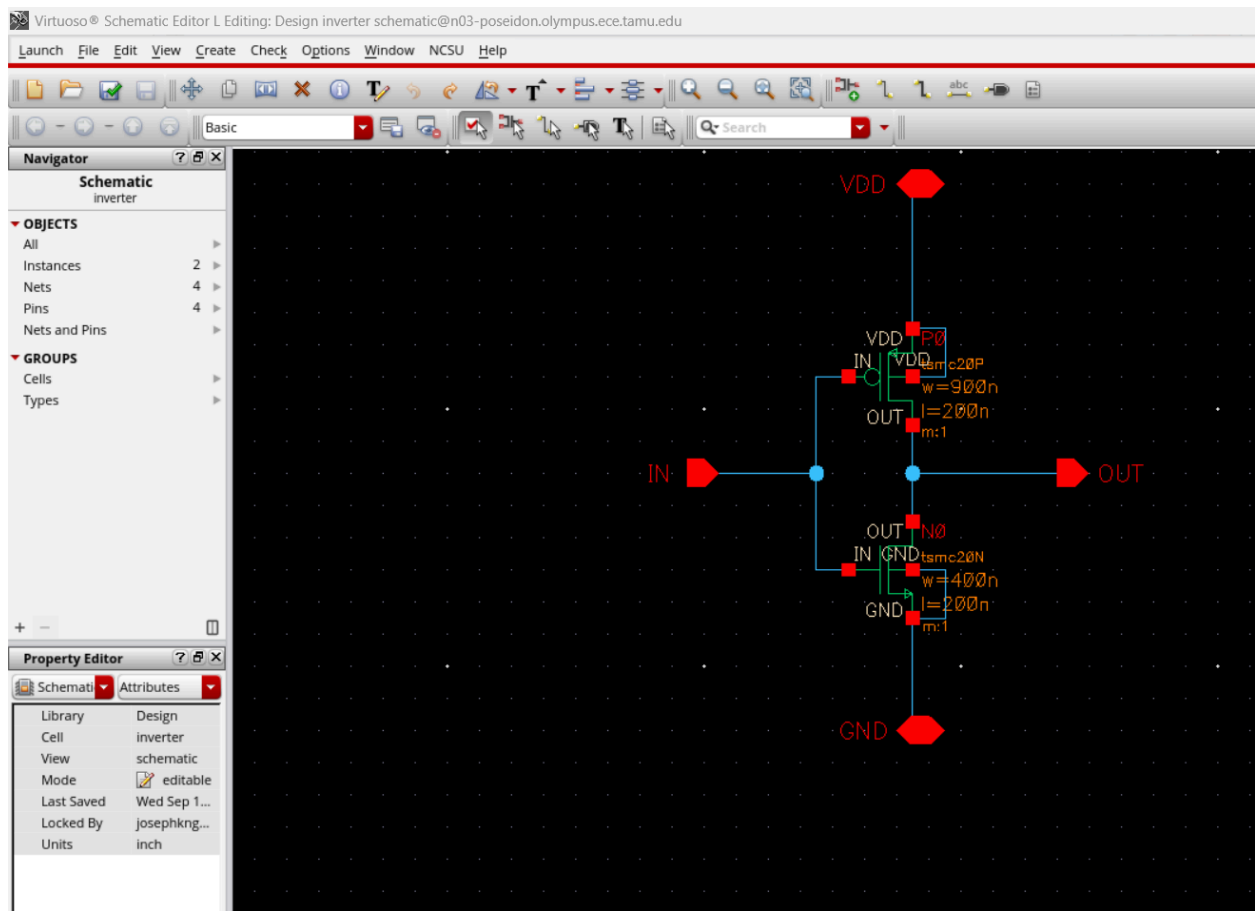

Inverter Symbol:

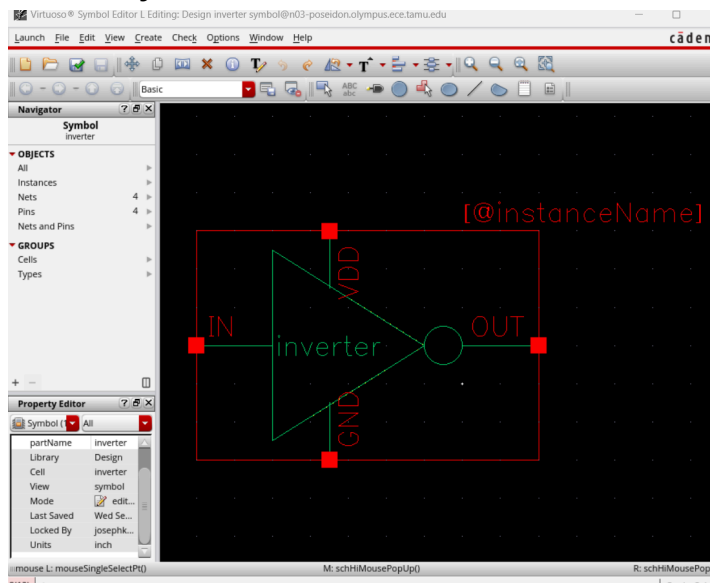

Inverter layout:

 

Inverter LVS:

Terminal correspondence points

N0	N2	GND
N2	N0	IN
N1	N1	OUT
N3	N3	VDD

Devices in the netlist but not in the rules:

pcapacitor

Devices in the rules but not in the netlist:


cap nfet pfet nmos4 pmos4

The net-lists match.


	layout	schematic
	instances	
un-matched	0	0
rewired	0	0
size errors	0	0
pruned	0	0
active	2	2
total	2	2
	nets	
un-matched	0	0
merged	0	0
pruned	0	0
active	4	4
total	4	4
	terminals	
un-matched	0	0
matched but		
different type	0	0
total	4	4

Probe files from /home/ugrads/j/josephknguyen02/ecen454_714/LVS/schematic


Nand2 schematic:

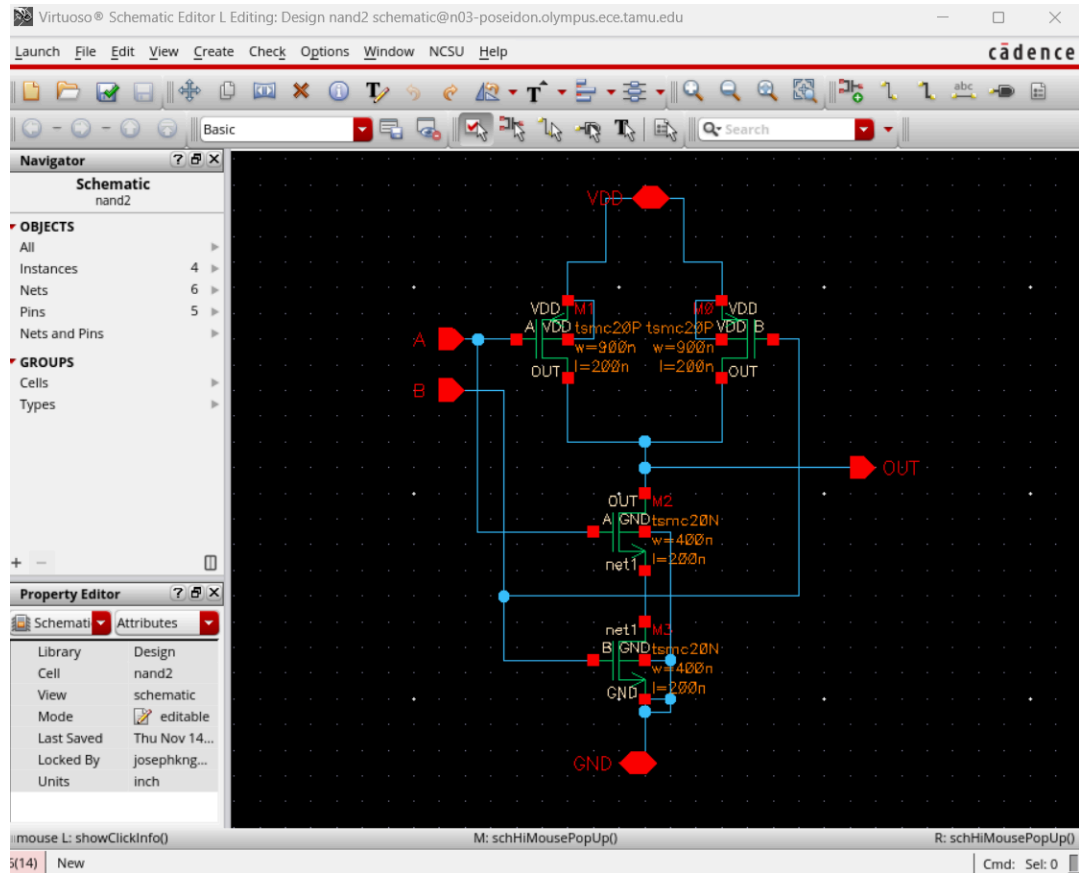

Nand2 symbol:

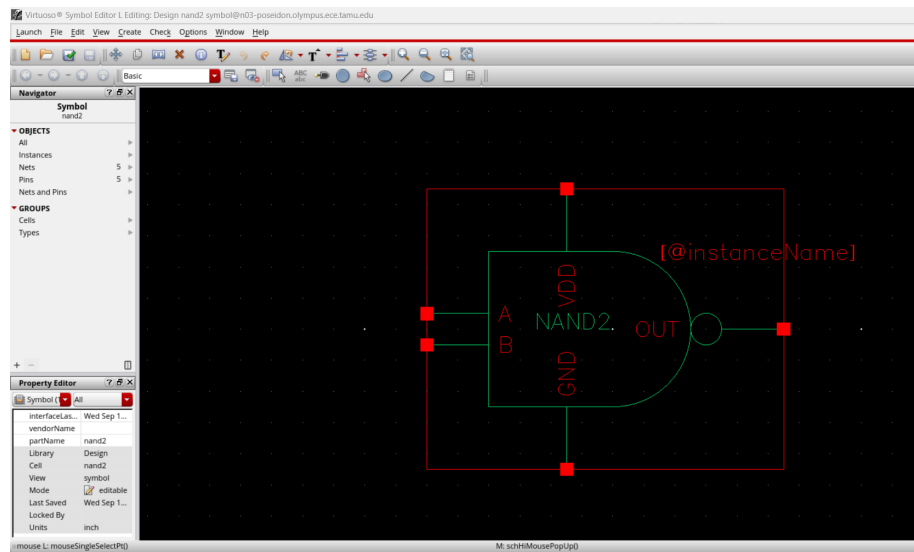

Nand2 layout:

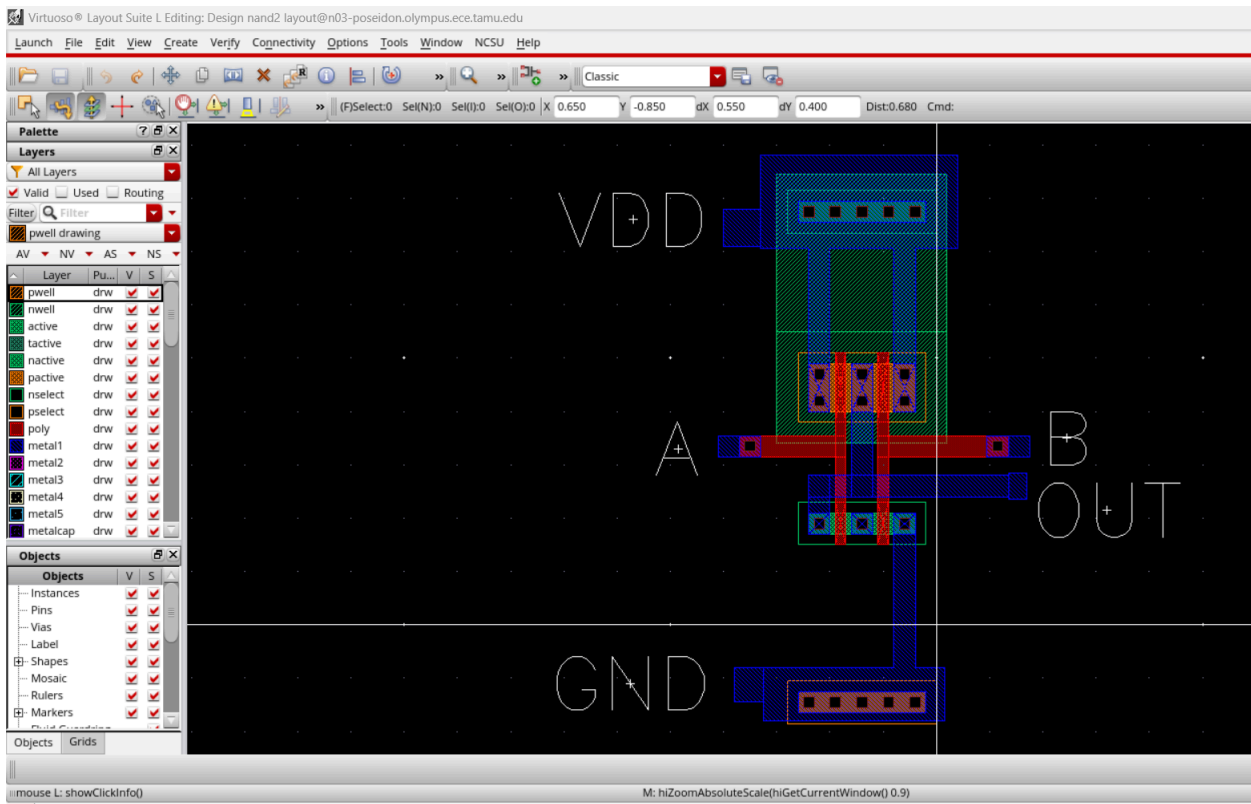

Nand2 LVS:

```
Terminal correspondence points
N4      N2      A
N3      N3      B
N1      N1      GND
N2      N4      OUT
N5      N0      VDD

Devices in the netlist but not in the rules:
pcapacitor pmos nmos

The net-lists match.


      layout schematic
      instances
un-matched      0      0
rewired          0      0
size errors      0      0
pruned           0      0
active           4      4
total            4      4

      nets
un-matched      0      0
merged           0      0
pruned           0      0
active           6      6
total            6      6


      terminals
un-matched      0      0
matched but
different type    0      0
total            5      5

Probe files from /home/ugrads/j/josephknguyen02/ecen454_714/LVS/schematic
```


Xor2 schematic:

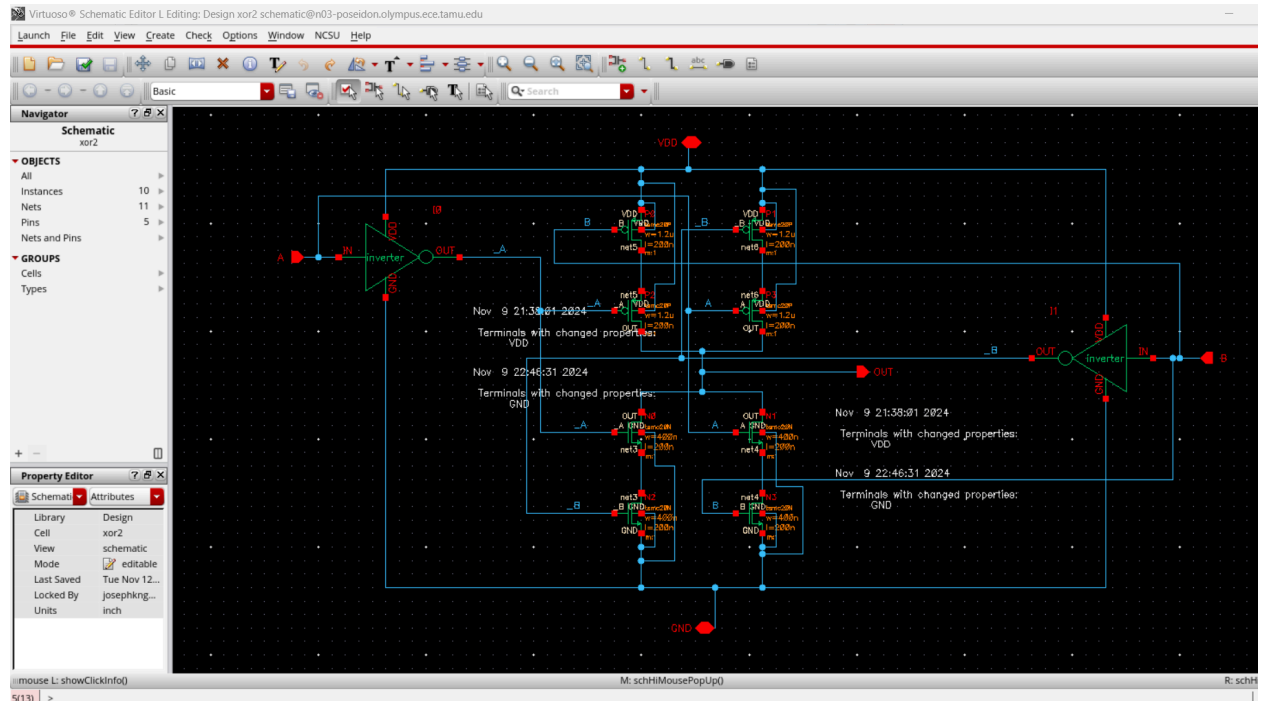

Xor2 symbol:

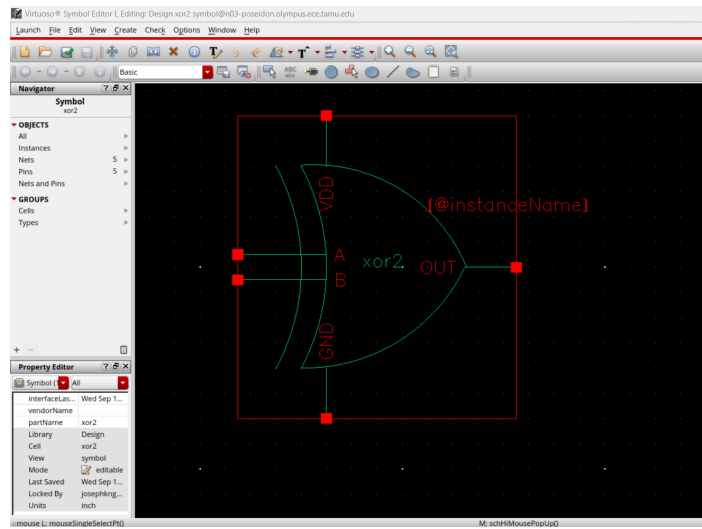

Xor2 layout:

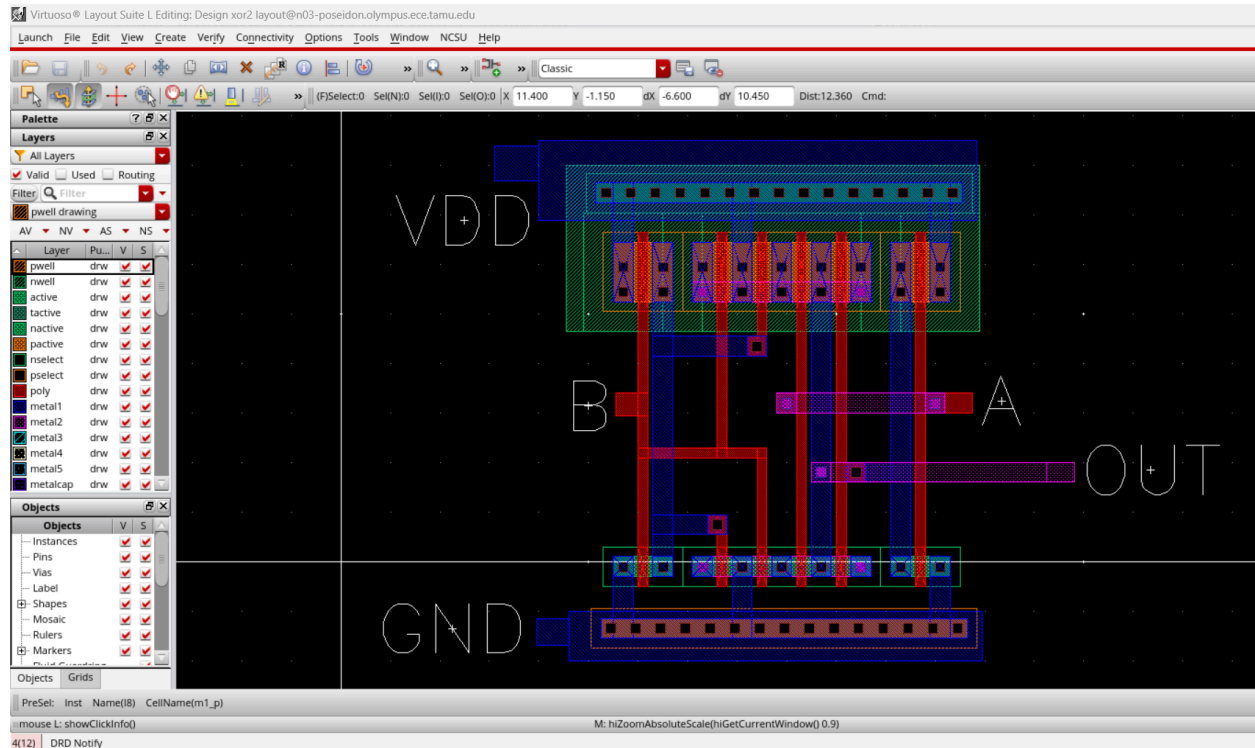

Xor2 LVS:

```

/home/ugrads/j/josephknguyen02/ecen454_714/LVS/si.out@n03-poseidon.olympus.ece.tamu.edu
File Edit View Help

N9      N0      A
N8      N1      B
N6      N4      GND
N7      N2      OUT
N10     N3      VDD

Devices in the netlist but not in the rules:
pcapacitor pmos nmos

The net-lists match.

          layout schematic
          instances
un-matched 0 0
rewired    0 0
size errors 0 0
pruned     0 0
active     12 12
total      12 12

          nets
un-matched 0 0
merged     0 0
pruned     0 0
active     11 11
total      11 11

          terminals
un-matched 0 0
matched but
different type 0 0
total      5 5

Probe files from /home/ugrads/j/josephknguyen02/ecen454_714/LVS/schematic
devbad.out:
netbad.out:

```