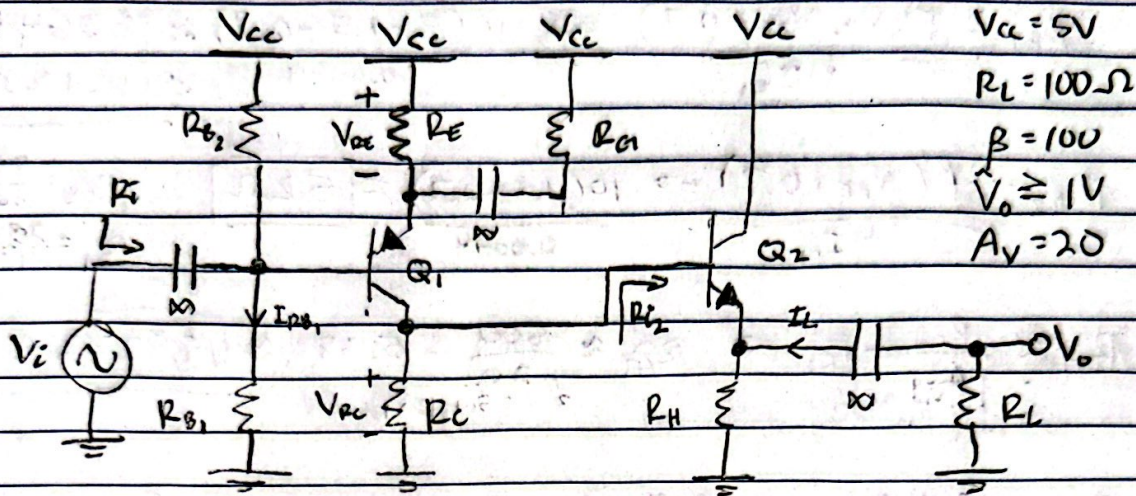


Lab 9 Calculations

Joseph
Nguyen

931006629



$$A_v = A_{v1} A_{v2}$$

$$\hat{V}_{be1} \ll V_T$$

$$I_{RE1} \gg I_{B1}$$

$$I_{C1} \gg I_{B2}$$

$$V_{RE} \gg 0.1V$$

$$* \text{Assume } A_{v2} \approx 1 + R_{C2} \gg R_L \Rightarrow A_{v2} = 20 + R_i = 1K\Omega$$

$$* \boxed{V_{RE} = 1.5V} \gg 0.1V \checkmark$$

$$* \boxed{V_0 = 1V} \geq 1V \checkmark$$

$$* V_{CE,sat} = 0.3V \geq 0.2V$$

$$* N = 10$$

$$V_{RC,max} = V_{CC} - \hat{V}_0 - V_{RE} - |V_{CE,sat}| \Rightarrow 5 - 1 - 1.5 - 0.3 = \boxed{2.2V}$$

$$\frac{V_{RC} - 0.7 - \hat{V}_0}{R_H} \geq \frac{\hat{V}_0}{R_L} \Rightarrow \frac{2.2 - 0.7 - 1}{R_H} \geq \frac{1}{100} \Rightarrow \underline{\underline{50 \geq R_H}}$$

$$\boxed{R_H = 50\Omega} \quad I_{C2} = \frac{V_{RC} - 0.7}{R_H} \Rightarrow \frac{2.2 - 0.7}{50} = \boxed{0.03A}$$

$$N \left(\frac{I_{C2}}{\beta} \right) \leq I_{C1} \leq \frac{\beta}{R_i} \left(\frac{N}{V_{BE} + 0.7} + \frac{N}{V_{CC} - V_{RE} - 0.7} + \frac{|R_{V1}|}{V_{RC}} \right)$$

$$\frac{0.03}{10} \leq I_{C1} \leq 0.1 \left(\frac{10}{2.2} + \frac{10}{2.8} + \frac{20}{2.2} \right) \Rightarrow 0.003 \leq I_{C1} \leq 0.0058$$

$$\boxed{I_{C1} = 0.0044A} = 4.4mA \quad R_C = \frac{V_{RC}}{I_{C1}} = \boxed{500\Omega}, R_E = \frac{V_{RE}}{I_{C1}} \approx \boxed{341\Omega}$$

$$① \quad R_{B1} = \frac{\beta(V_{CC} - V_{RE} - 0.7)}{NI_{C1}} \Rightarrow \frac{10(5 - 1.5 - 0.7)}{0.0044} \approx \boxed{6364 \Omega} \approx \boxed{6.4 k\Omega}$$

$$R_{B2} = \frac{\beta(V_{RE} + 0.7)}{NI_{C1}} \Rightarrow \frac{10(1.5 + 0.7)}{0.0044} \approx \boxed{5 k\Omega}$$

$$r_{e2} = \frac{25}{30} = 0.83 \Omega$$

$$r_{e1} = \frac{25}{44} = 5.68 \Omega$$


$$R_G \approx \frac{R_C}{|A_v|} - r_{e1} \Rightarrow R_{C1} \approx \frac{500}{20} - 5.68 \approx \boxed{19.32 \Omega \approx 20 \Omega}$$

$$A_{v2} = \frac{R_H \parallel R_L}{r_{e2} + (R_H \parallel R_L)} \Rightarrow \frac{50 \parallel 100}{0.83 + (50 \parallel 100)} \approx 0.9756 \approx 1 \checkmark$$


$$R_{i2} = (\beta + 1)(r_{e2} + (R_H \parallel R_L)) \Rightarrow (101)(0.8333 + 33.33) \approx 3450 \Omega$$

$$3450 \Omega \gg 500 \checkmark$$

Final circuit:

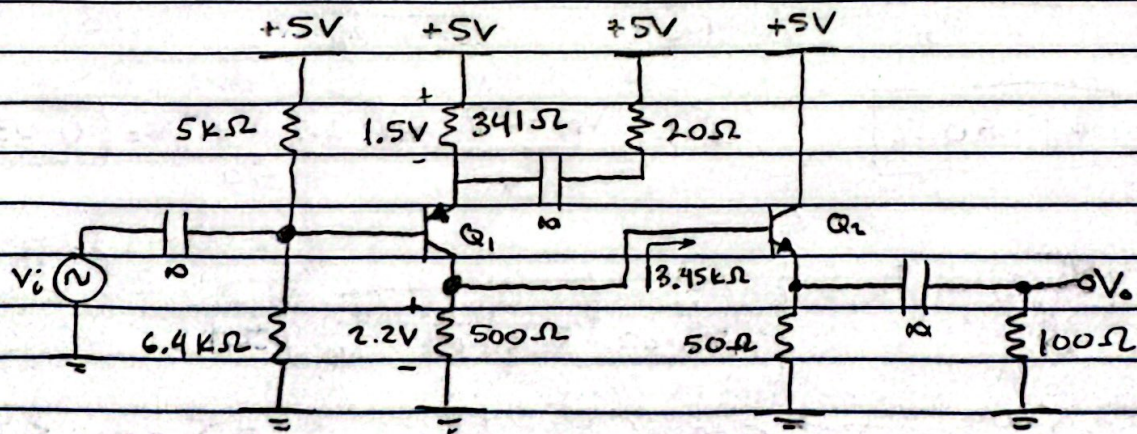

Schematic:

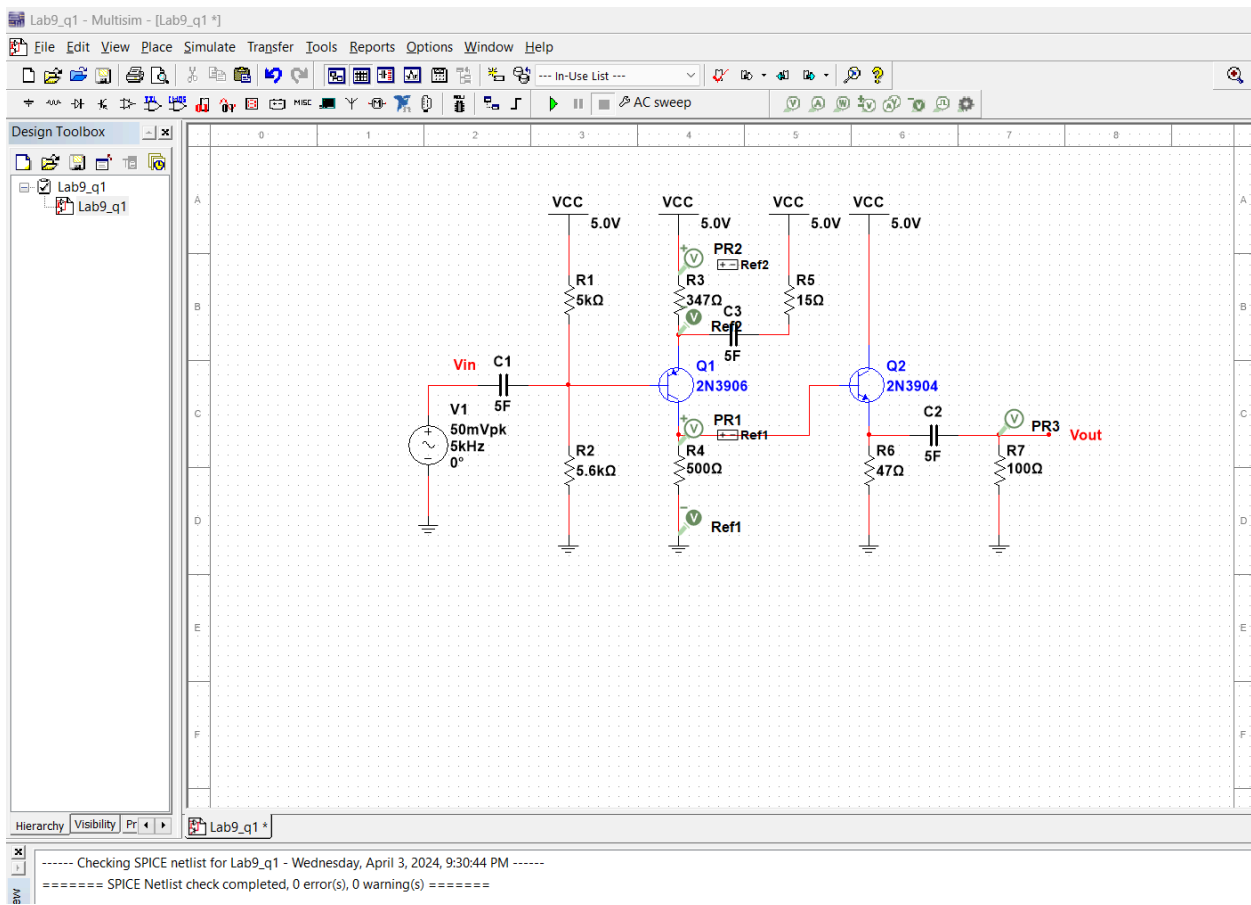


Here is a picture of the schematic that I used for the simulations. Some changes I made were for R_{B1} and R_G , I adjusted the values to 5.6k and 15 respectively since the DC operating point and A_v was slightly off. I also used 347 for R_E and 47 for R_H , in order to make it more convenient to use for the lab.

DC Operating Point:


Lab9_q1		
DC Operating Point Analysis		
Printing Time: Wednesday, April 3, 2024, 5:07:14 PM		
Variable	Operating point value	
1 V(5) - V(0) V(PR1)	2.12329	
2 V(vcc) - V(3) V(PR2)	1.54712	
3 V(vout) V(PR3)	0.00000e+00	
4 I(Q1[IC])	4.43348 m	
5 I(Q2[IC])	28.77482 m	

For the DC Operating point, we can see that the values for V_{RC} (2.12V), V_{RE} (1.54V), I_{C1} (4.43mA), and I_{C2} (28.7mA) are consistent with the calculated values.

A_v and R_i magnitude plots:

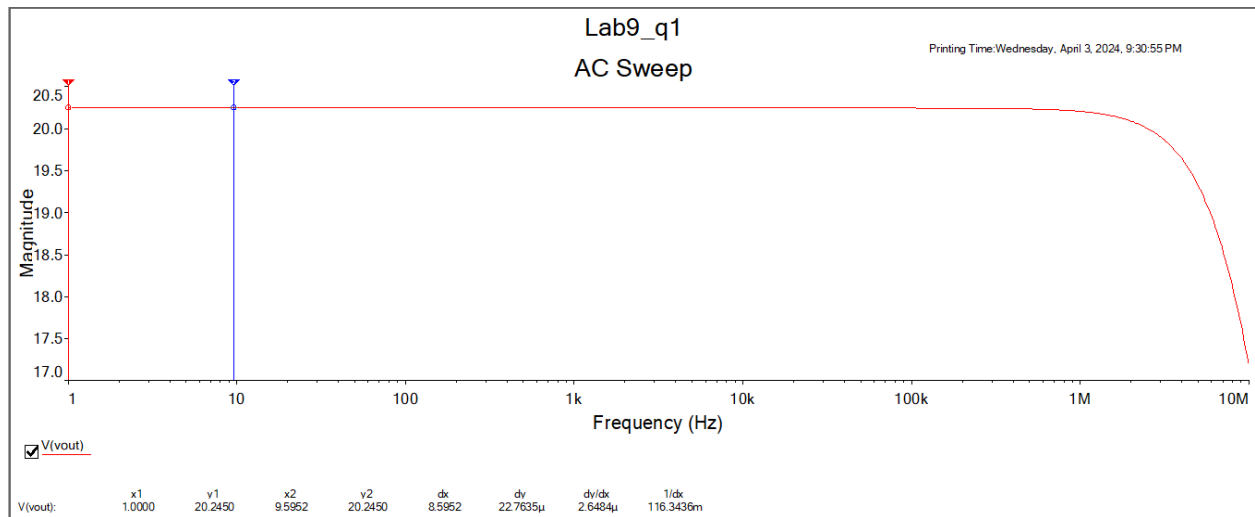


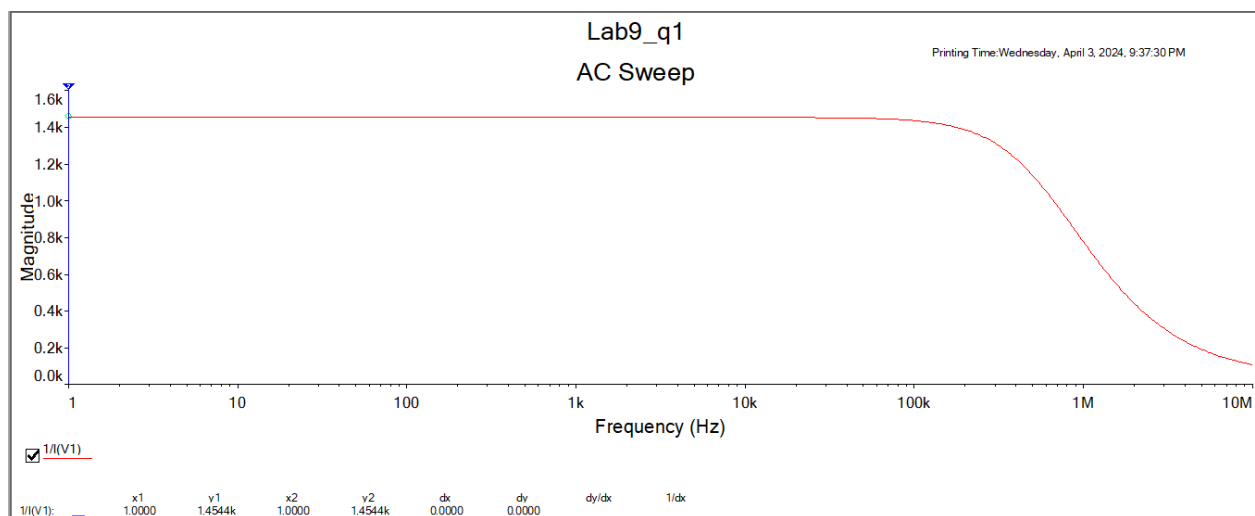Here we can see that the magnitude of A_v for this circuit is 20.25 which has little to no difference to the parameter.



Here we can see that the input resistance is 1.45k which satisfies the parameter for $R_i \geq 1k$.

Time domain waveform:

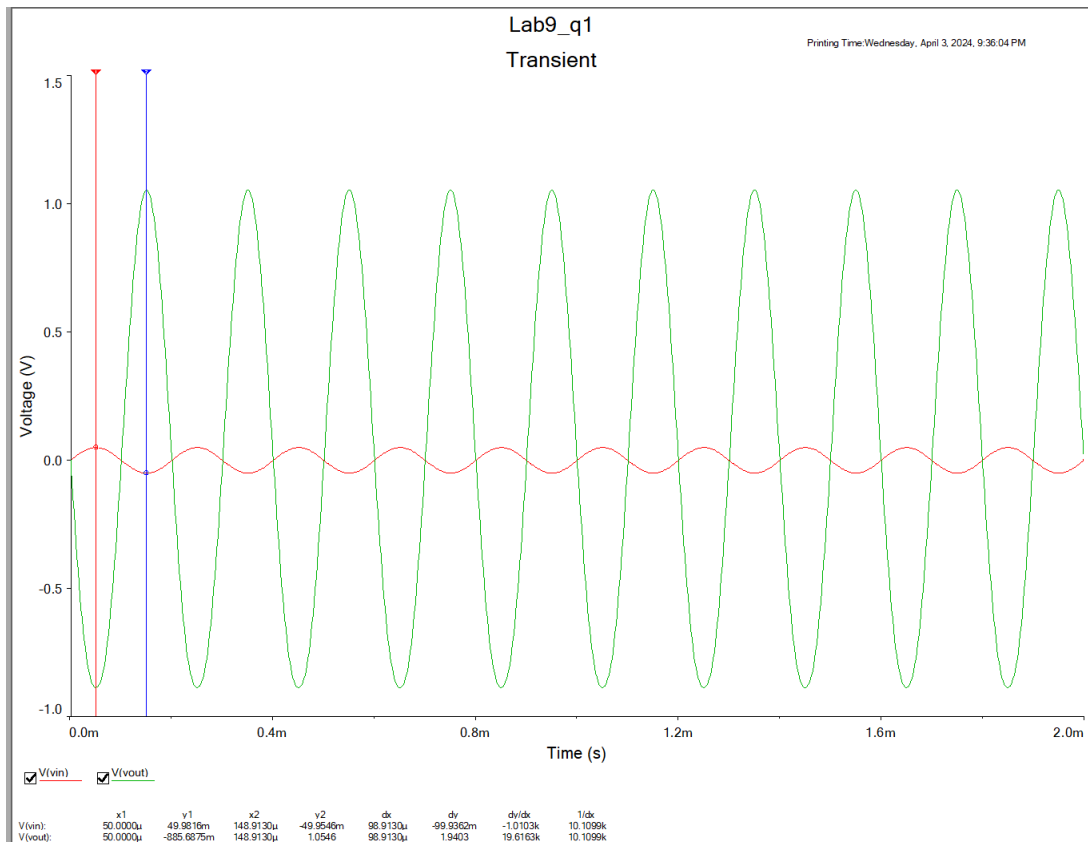

Here is a photo of the transient plot which shows the output voltage amplitude at 1.05V.

THD:

Printing Time: Wednesday, April 3, 2024, 9:35:08 PM

1	Fourier analysis for V(vou				
2	DC component:	0.0388689			
3	No. Harmonics:	10			
4	THD:	4.4047 %			
5	Grid size:	256			
6	Interpolation Degree:	1			
7					
8	Harmonic	Frequency	Magnitude	Phase	Norm. Mag
9	0	0	0.0388689	0	0.0394844
10	1	5000	0.984412	179.98	1
11	2	10000	0.0416922	-90.117	0.0423524
12	3	15000	0.0112555	-179.91	0.0114337
13	4	20000	0.00340069	89.7275	0.00345454
14	5	25000	0.00167415	0.112637	0.00170066
15	6	30000	0.000727165	-90.335	0.000738679
16	7	35000	0.000496544	-179.99	0.000504406
17	8	40000	0.000164716	89.6648	0.000167324
18	9	45000	0.000166168	0.0371392	0.000168799
19	10	50000	2.12207e-05	-91.555	2.15568e-05
20					

Here, the THD is 4.4% which satisfies the parameter for THD <= 5%.