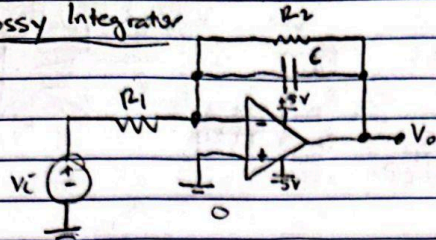


# Calculations:

Joseph  
Nguyen

## Lab 5 calculations.

### ① Lossy Integrator



$$R_2 \parallel Z_c = \frac{R_2}{sR_2C + 1}$$

$$\frac{0 - V_i}{R_1} + \frac{(0 - V_o)(1 + sR_2C)}{R_2} = 0$$

$$\frac{-V_i}{R_1} = \frac{V_o}{R_2} (1 + sR_2C)$$

$$V_o = \frac{-\frac{R_2}{R_1} V_i}{1 + sR_2C}$$


### ②

$$\frac{V_o}{V_i} = -22, R_2 = 22 \text{ k}\Omega, C = 220 \text{ nF}$$


$$\frac{V_o}{V_i} = -\frac{R_2}{R_1} \Rightarrow -22 = -\frac{22 \text{ k}\Omega}{R_1} \Rightarrow R_1 = 1 \text{ k}\Omega$$

$$\omega_{3-dB} = \frac{1}{R_2C} \approx 206.6 \quad \omega = 2\pi f \quad \frac{206.6}{2\pi} = f$$
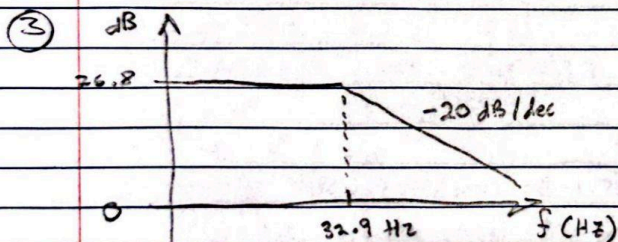
$$f_{3-dB} \approx 32.9 \text{ Hz} \quad H(s) = -22 \left[ \frac{1}{1 + \frac{s}{2\pi 32.9}} \right]$$



Magnitude Bode Plot

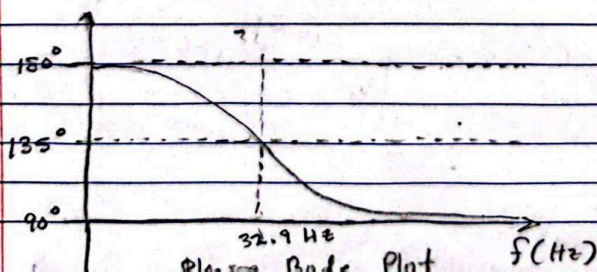

Phase Bode Plot




④  $V_i(t) = 0.5 \sin(2\pi 1000t)$ ,  $H(s) = -22 \left[ \frac{1}{1 + \frac{s}{2\pi 32.9}} \right]$

$$|H(2\pi 1000)| = 22 \left[ \frac{1}{\sqrt{1 + \left(\frac{2\pi 1000}{2\pi 32.9}\right)^2}} \right] \approx 0.7234$$


$$\angle H(2\pi 1000) = -\pi - \tan^{-1}\left(\frac{\omega}{\omega_0}\right) = -\pi - \tan^{-1}\left(\frac{1000}{32.9}\right) \approx -4.68 \text{ rad}$$

$$V_o(t) = (0.7234)(0.5 \sin(2\pi 1000t - 4.68))$$
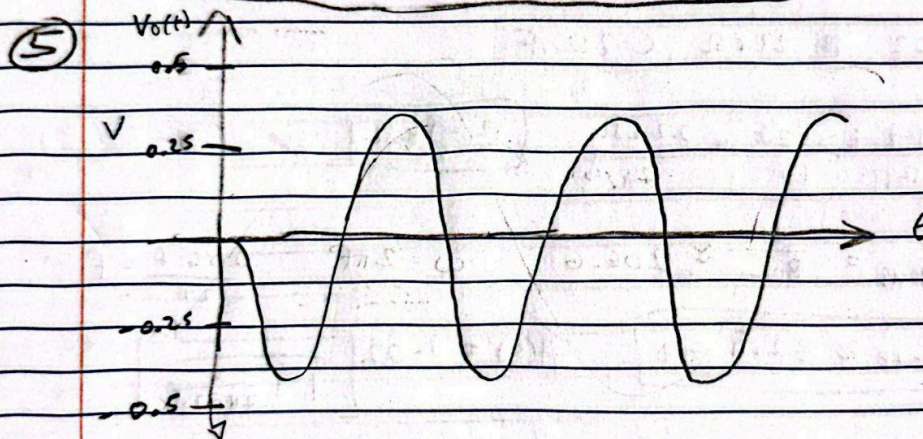
$$\boxed{V_o(t) = 0.3617 \sin(2\pi 1000t - 4.68)}$$



### Pseudo Differentiator

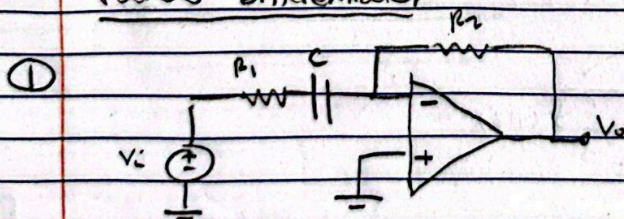

$$V_o = -\frac{R_2}{R_1 + \frac{1}{sC}} V_i$$

$$V_o = -\frac{sR_2C}{sR_2C + 1} V_i$$

$$= -\frac{R_2}{R_1} \left( \frac{sC}{sC + \frac{1}{R_1}} \right) V_i$$

$$\boxed{V_o = -\frac{R_2}{R_1} \left( \frac{s}{s + \frac{1}{R_1C}} \right) V_i}$$



# Lab 5

## Pseudo Differential

(2)



$$\frac{V_o}{V_i} = -22, R_1 = 1 \text{ k}\Omega, C = 33 \text{ nF}$$

$$\frac{V_o}{V_i} = -\frac{R_2}{R_1} \Rightarrow -22 = \frac{R_2}{1 \text{ k}\Omega} \quad \boxed{R_2 = 22 \text{ k}\Omega}$$

$$\omega_{3dB} = \frac{1}{R_1 C} \approx 30303 \text{ rad/s} \approx 2\pi 4822.9 \text{ rad/s}$$

$$f = \frac{\omega}{2\pi} \approx \boxed{4822.9 \text{ Hz}} \quad H(s) = -22 \left[ \frac{s}{s + 2\pi 4822.9} \right]$$

(3)

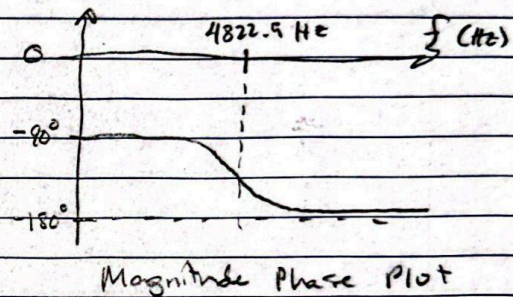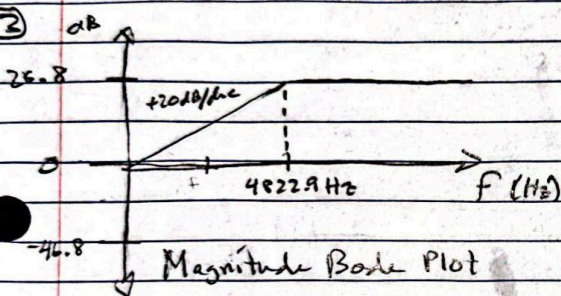

(4)


$$V_i(t) = 0.1 \sin(2\pi 1000 t)$$

$$|H(2\pi 1000)| = \frac{22}{\sqrt{1 + \left(\frac{4822.9}{1000}\right)^2}} \approx 4.47, \angle H(2\pi 1000) = -\pi + \tan^{-1}\left(\frac{4822.9}{1000}\right) \approx -1.78 \text{ rad}$$

$$V_o(t) = (4.47)(0.1 \sin(2\pi 1000 t - 1.78))$$

$$\boxed{V_o(t) = 0.447 \sin(2\pi 1000 t - 1.78)}$$

(5)

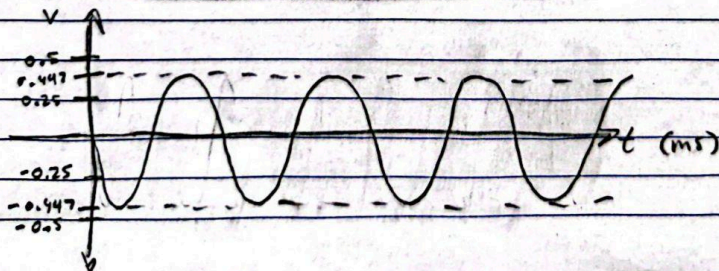




# Finite GBPW Limitations

$$\frac{V_o}{V_i} = \frac{G_o}{1 + \frac{s}{\omega_o}} \quad G_o = 1 + \frac{R_2}{R_1}$$

$$\omega_o = \frac{\omega_t}{G_o}$$

①

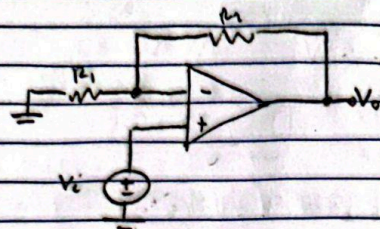

$$G_o = 23: \quad 23 = 1 + \frac{R_2}{1k}$$

$$22 = \frac{R_2}{1k} \Rightarrow R_2 = 22k\Omega$$

$$G_o = 57: \quad 57 = 1 + \frac{R_2}{1k}$$

$$56 = \frac{R_2}{1k} \Rightarrow R_2 = 56k\Omega$$

$$G_o = 83: \quad 83 = 1 + \frac{R_2}{1k}$$

$$82 = \frac{R_2}{1k} \Rightarrow R_2 = 82k\Omega$$

$$\omega_t = 1.2MHz \cdot 2\pi$$

$$2\pi \cdot 1.2MHz = G_o \omega_o$$

②

$$\omega_o = \frac{\omega_t}{1 + \frac{R_2}{R_1}} = \frac{1.2MHz \cdot 2\pi}{1 + \frac{R_2}{R_1}}$$

$$\text{for } G_o = 23: \quad \omega_o = \frac{1.2MHz \cdot 2\pi}{23} = 2\pi 52174 \text{ rad/s}$$

$$\left| \frac{V_o}{V_i} \right| = 23 \left[ \frac{1}{1 + \frac{s}{2\pi 52174}} \right]$$

$$\text{for } G_o = 57: \quad \omega_o = \frac{1.2MHz \cdot 2\pi}{57} = 2\pi 21053 \text{ rad/s}$$


$$\left| \frac{V_o}{V_i} \right| = 57 \left[ \frac{1}{1 + \frac{s}{2\pi 21053}} \right]$$

$$\text{for } G_o = 83: \quad \omega_o = \frac{2\pi \cdot 1.2MHz}{83} \approx 2\pi 14458 \text{ rad/s}$$


$$\left| \frac{V_o}{V_i} \right| = 83 \left[ \frac{1}{1 + \frac{s}{2\pi 14458}} \right]$$



# Lab 5

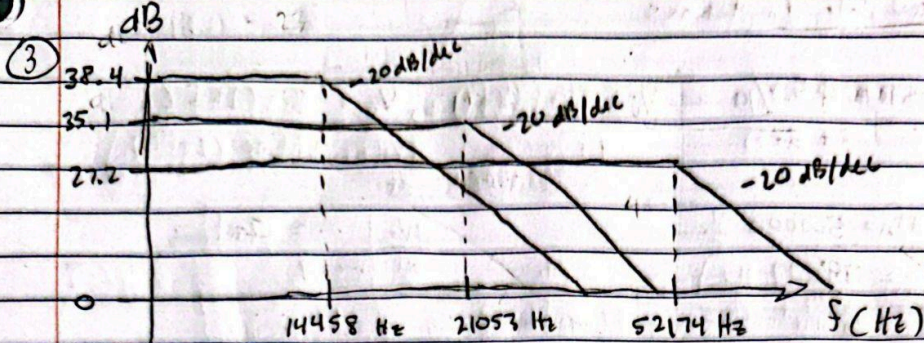

Magnitude Bode Plot


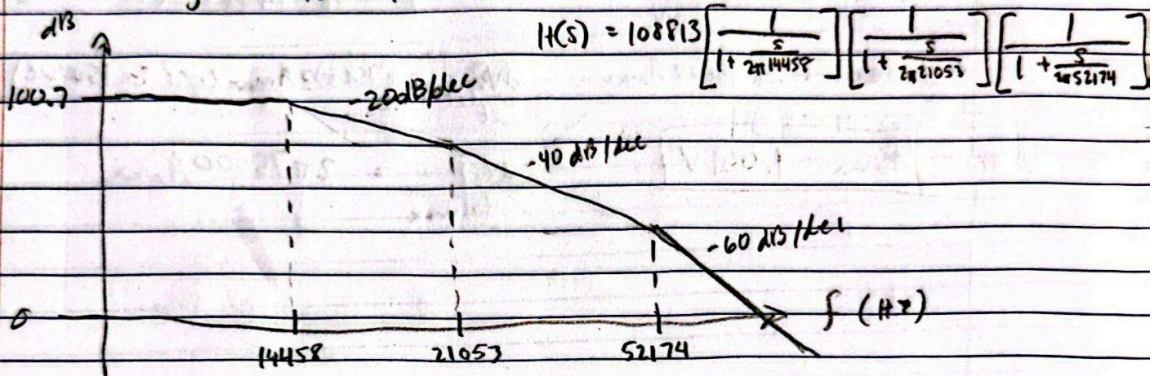


Magnitude Bode plot

## Slew Rate Limitations

$$V_o = V_{i1}, \quad V_P = V_N$$

①

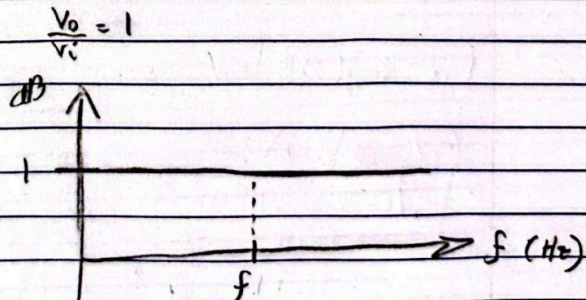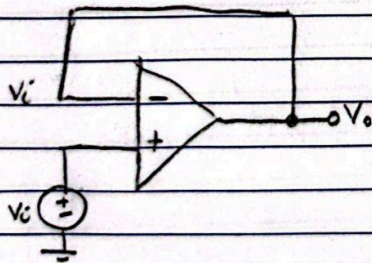

Magnitude Bode Plot



### Slew Rate Limitations

(2)

$$SR = 0.5 \text{ V}/\mu\text{s} \quad V_o = \sin(2\pi f t), \quad V_o = \sin(2\pi f t)$$

$$\frac{dV_o}{dt} = 2\pi f \cos(2\pi f t)$$

$$2\pi f_{\max} = 500000 \text{ V}$$

$$\left. \frac{dV_o}{dt} \right|_{\max} = 2\pi f_{\max}$$

$$\boxed{f = 79577 \text{ Hz}}$$

(3)

$$SR = 0.5 \text{ V}/\mu\text{s} \quad f = 75 \text{ kHz}, \quad V_o = A_{\max} \sin(2\pi 75000 t)$$


$$500000 = 2\pi 75000 A_{\max}$$

$$\frac{dV_o}{dt} = 2\pi 75000 A_{\max} \cos(2\pi 75000 t)$$


$$\boxed{A_{\max} = 1.061 \text{ V}}$$

$$\left. \frac{dV_o}{dt} \right|_{\max} = 2\pi 75000 A_{\max}$$


## Circuit Schematics: Lossy-Integrator:

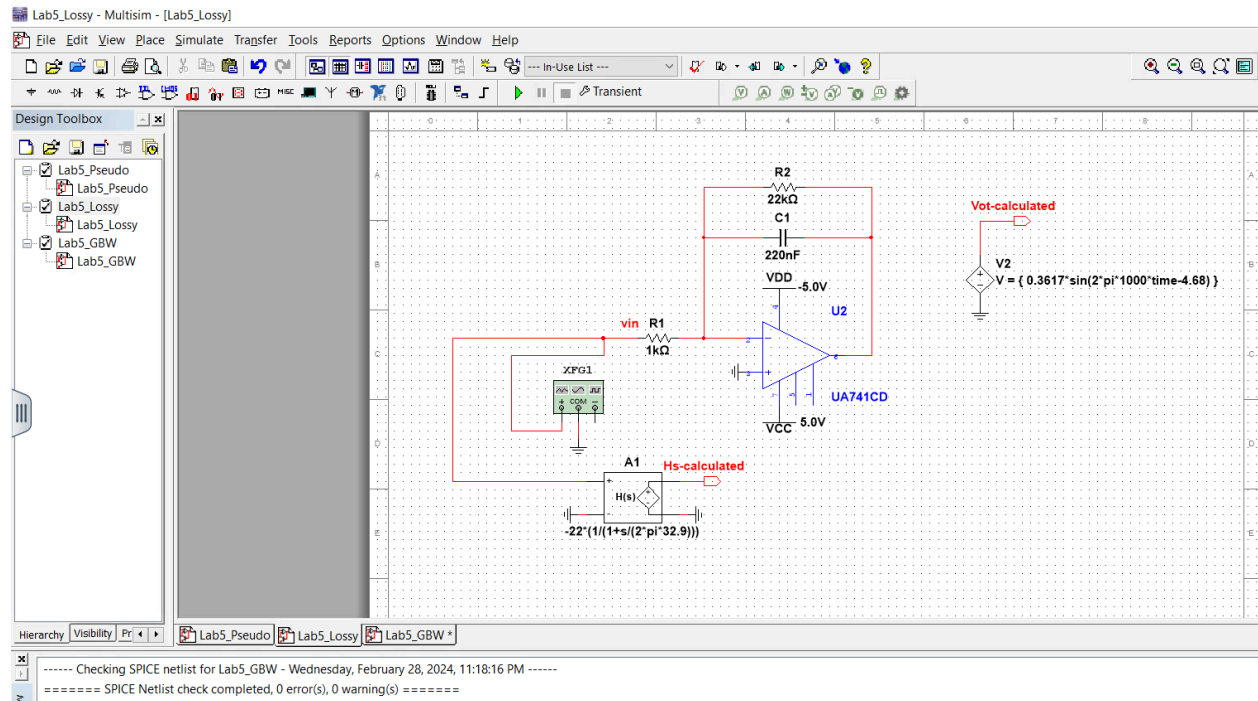


## Pseudo Differentiator:

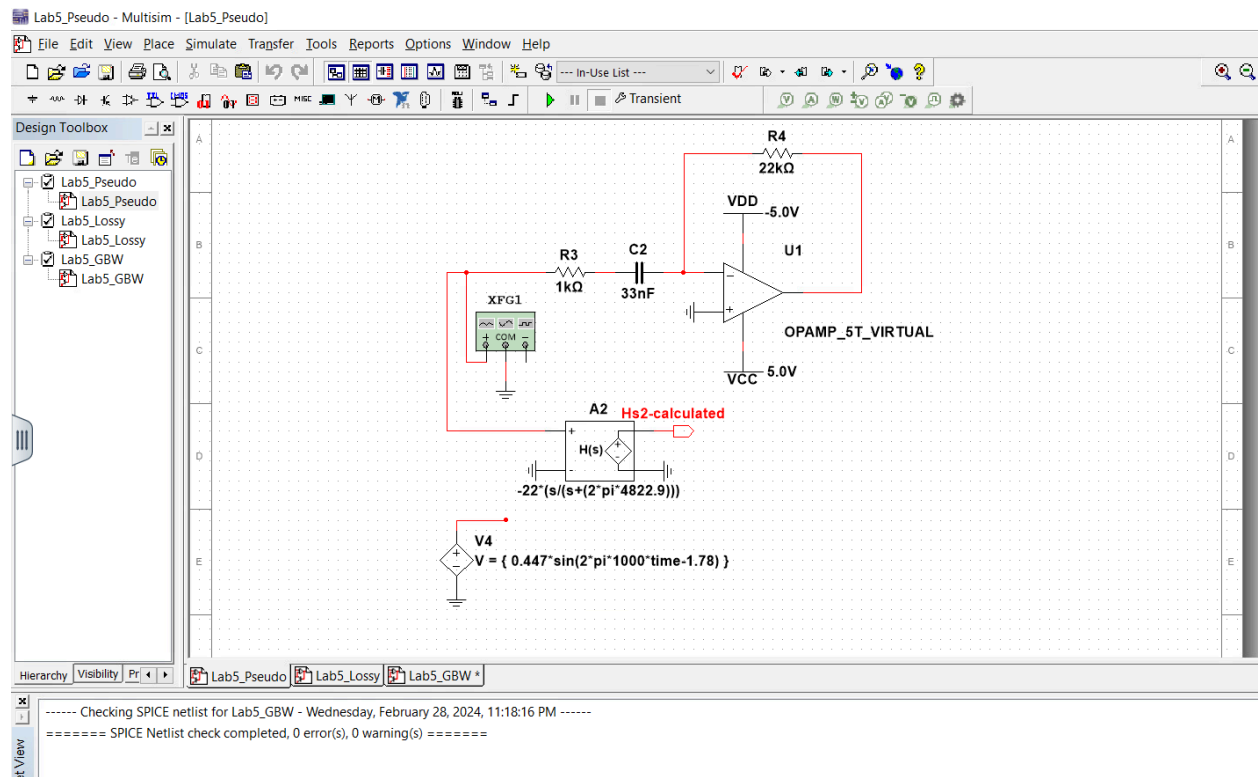

## Non-inverting Amplifier:

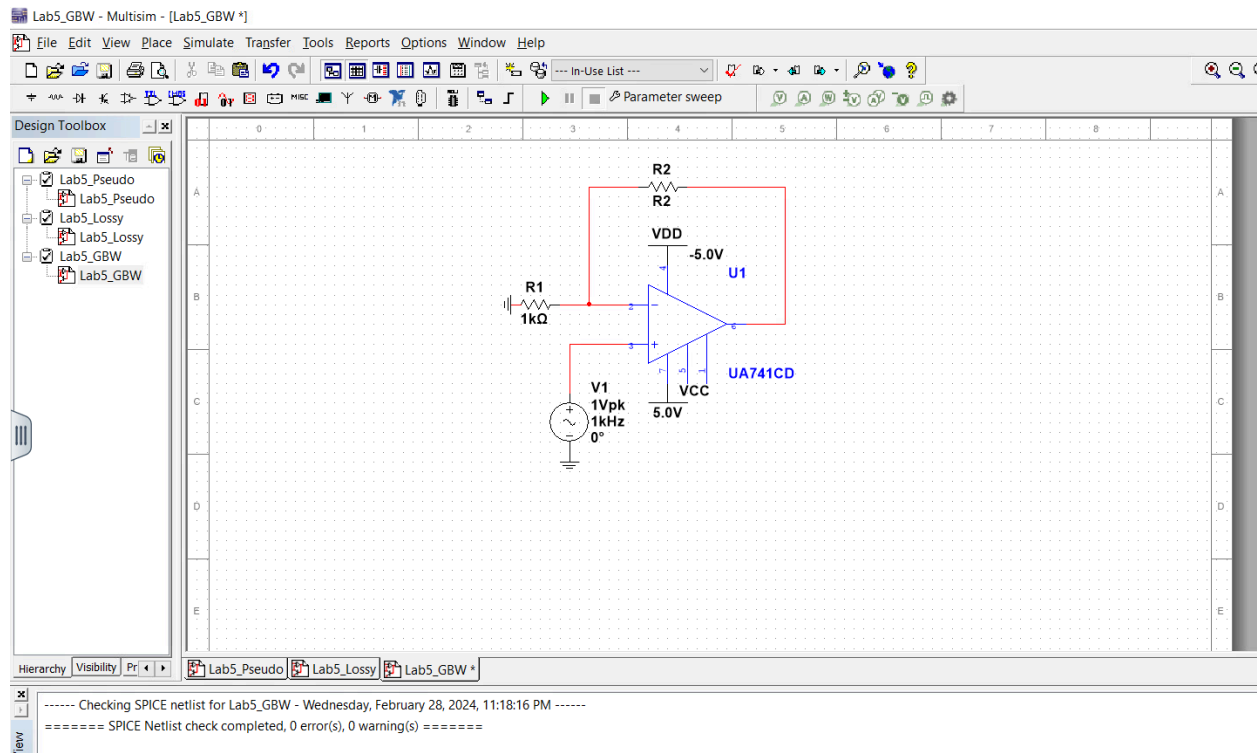

## Buffer Amplifier:


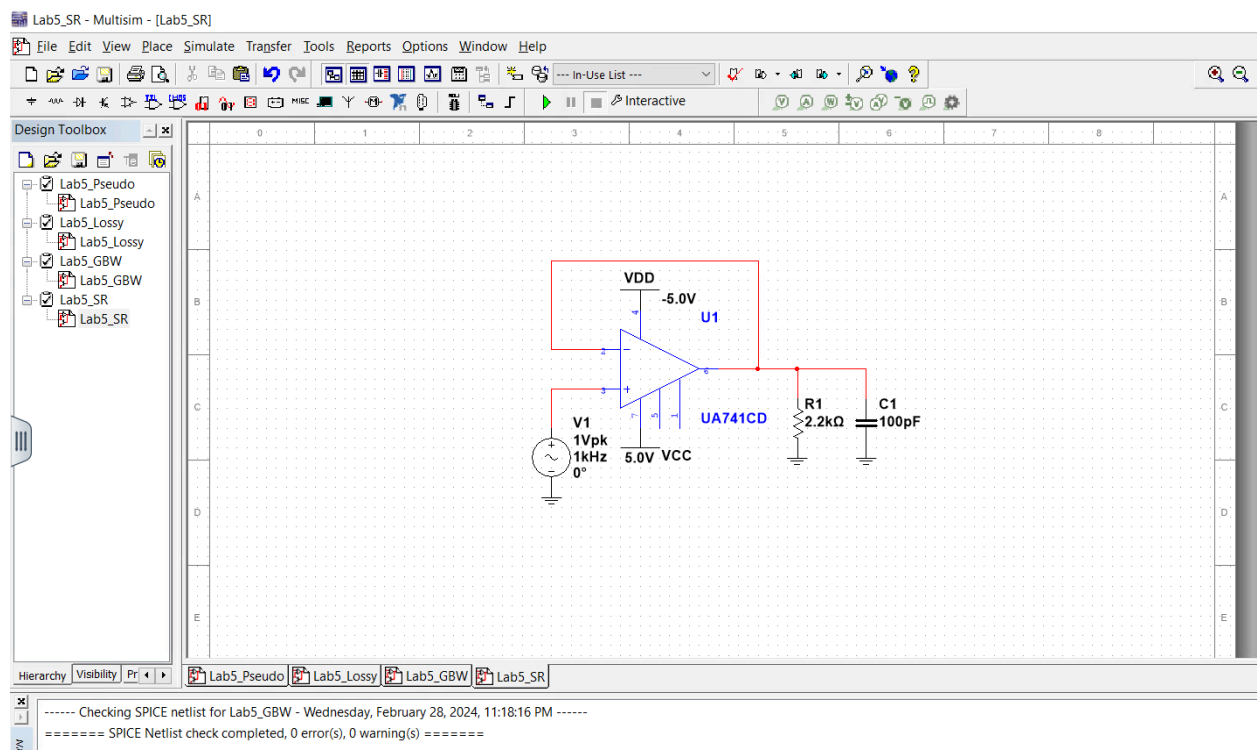




## Simulations:


### Lossy Integrator

### Bode Plots:

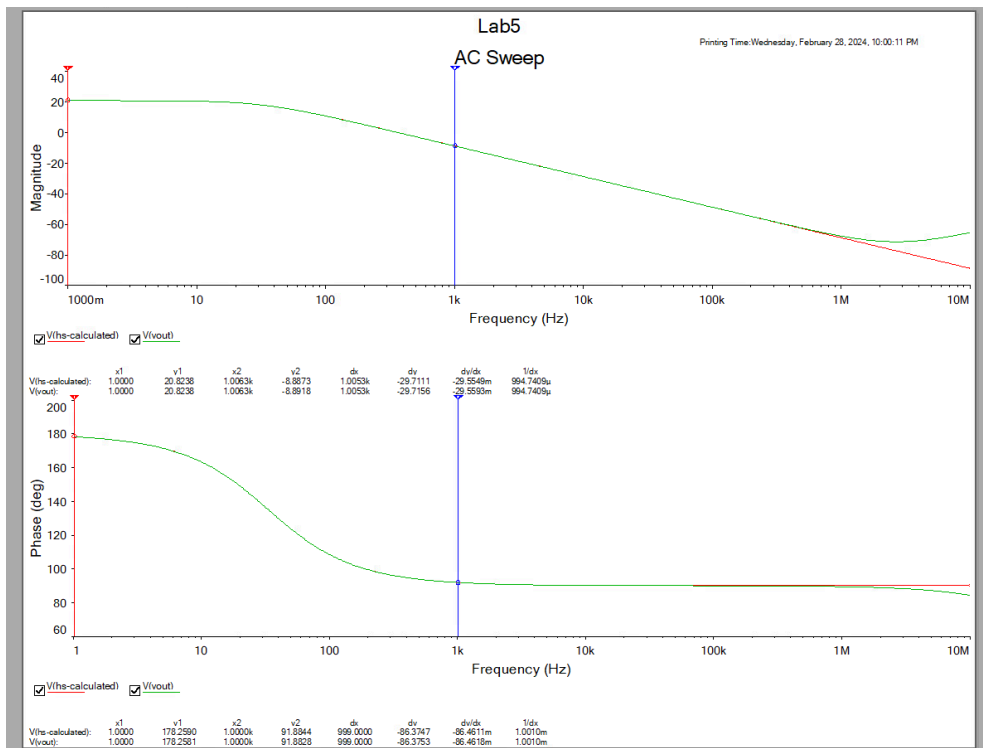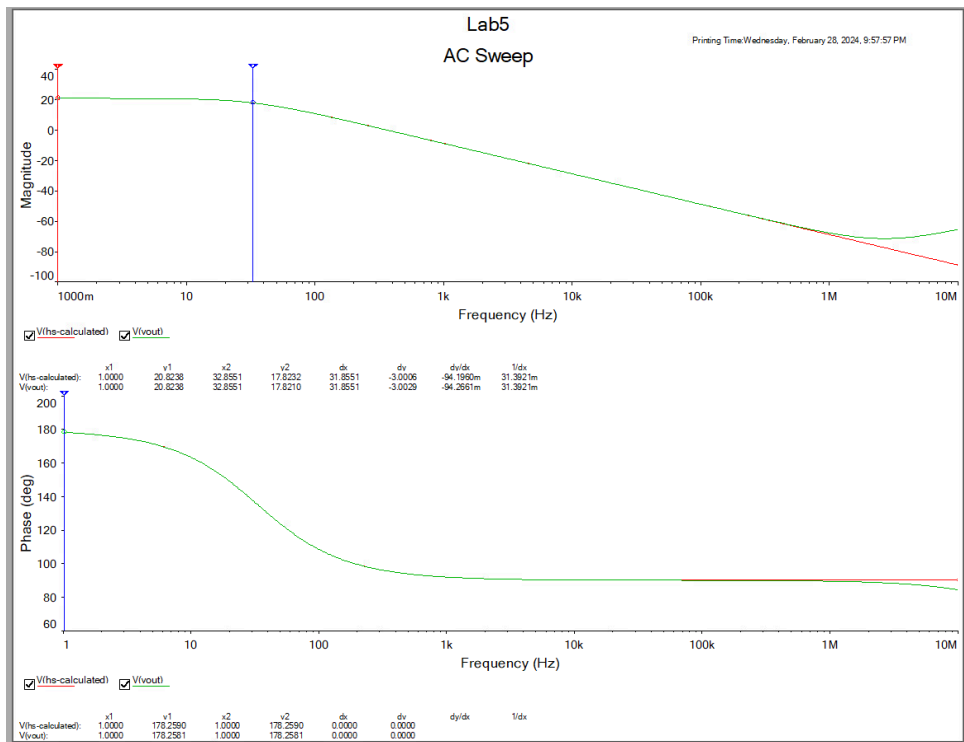


Here we can see that the  $f_{3-dB}$  is at 32.9 Hz, and that the low frequency gain is 20.8 dB. The magnitude and phase at 1 kHz is -8.89 dB and 91.9° respectively.

Transient Plots:

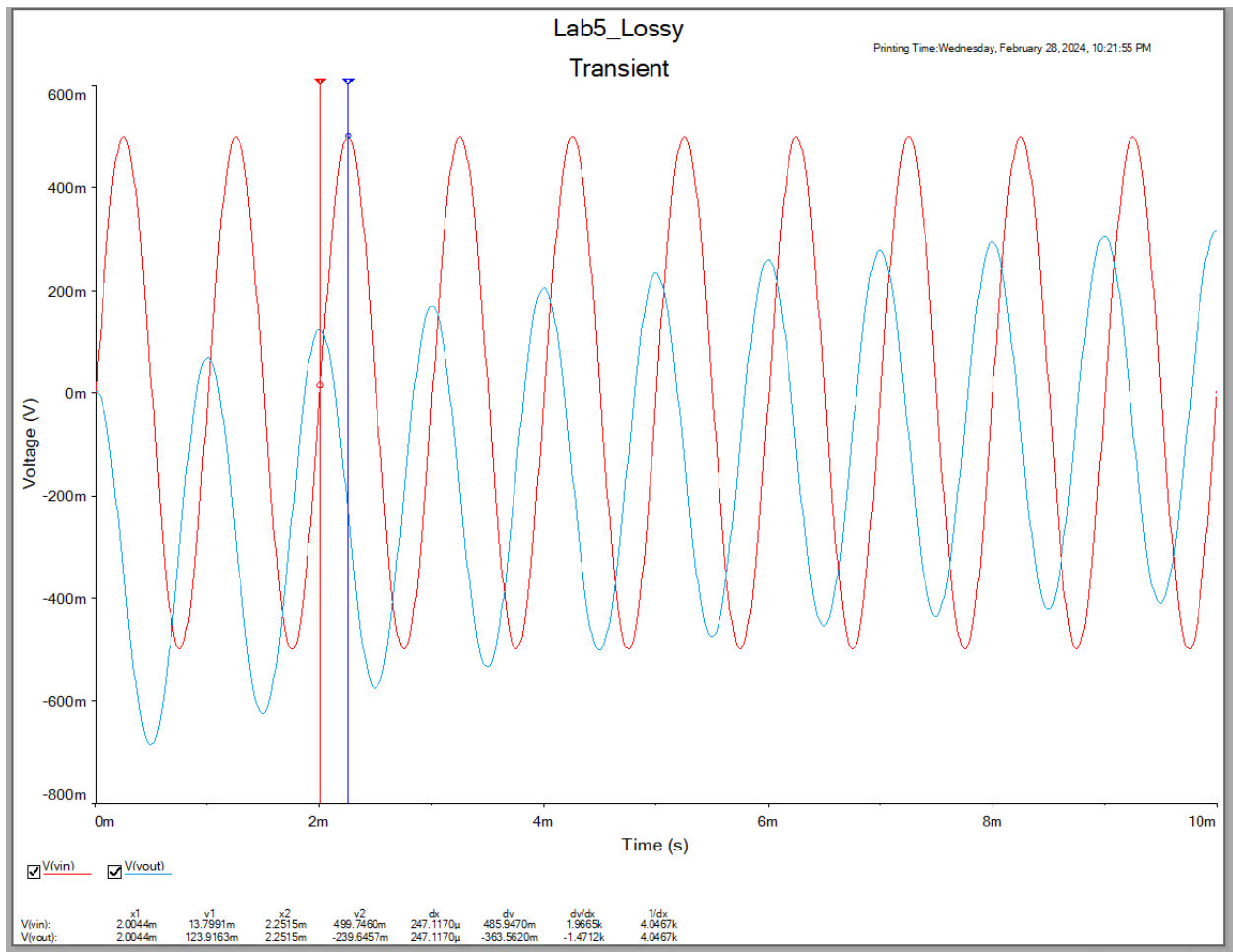

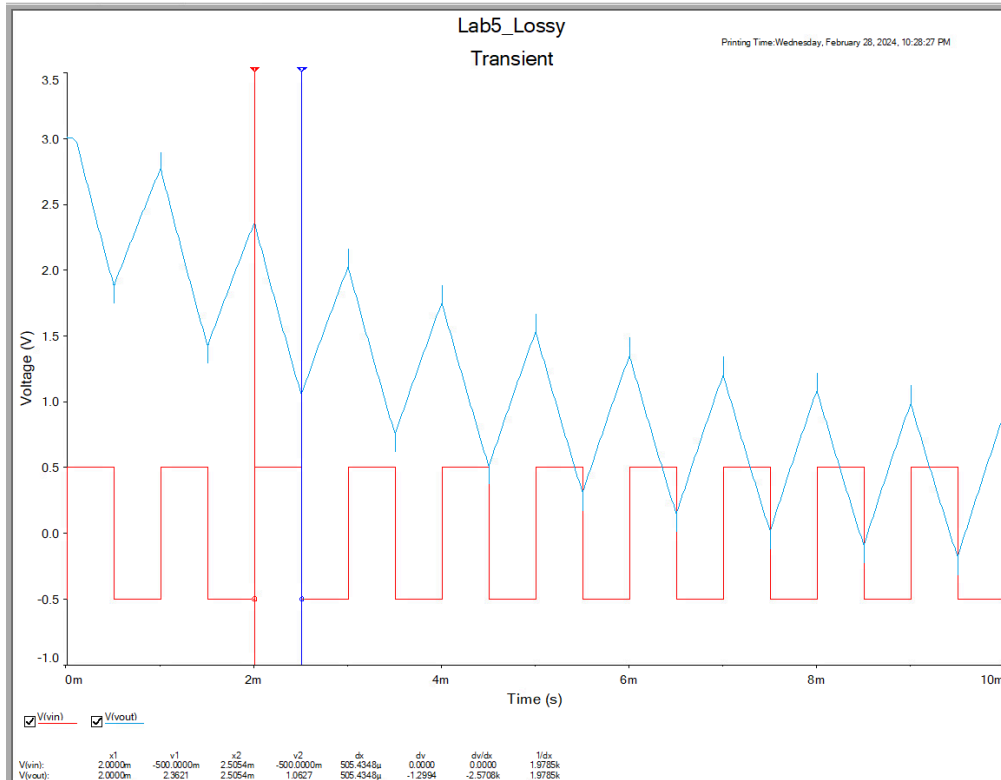The phase difference calculated is  $91.5^\circ$  or 1.6 rads.







The  $V_{pp}$  for  $V_{in}$  and  $V_{out}$  are 1 V and 1.3 V respectively

### Pseudo Differentiator

Bode Plots:

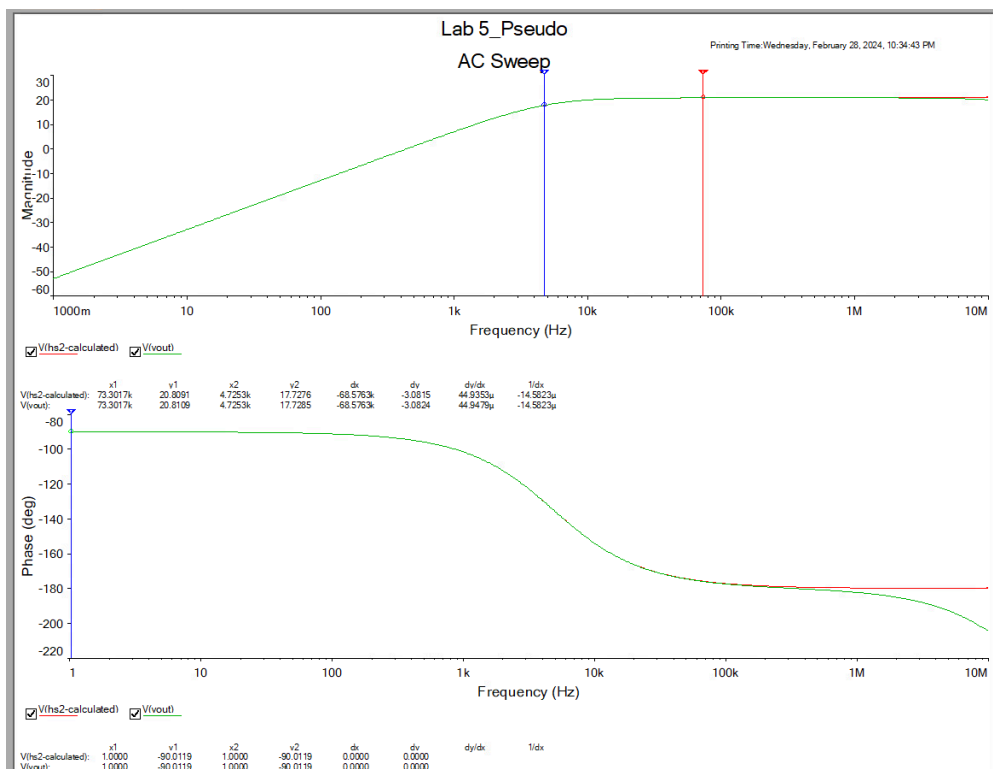


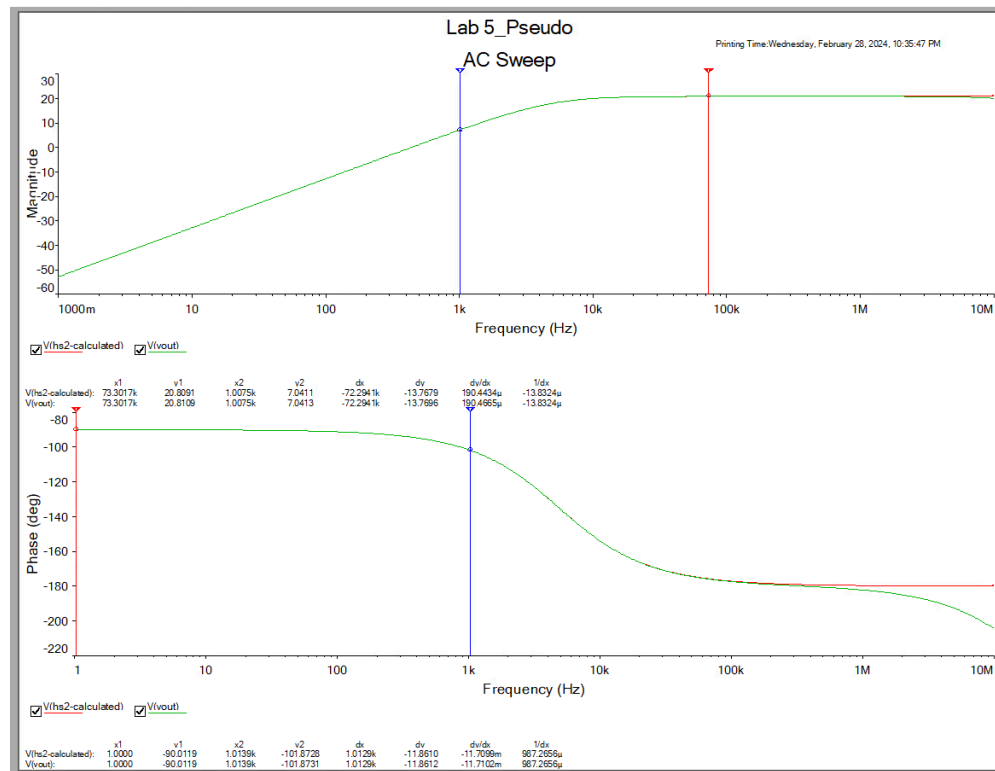


The  $f_{3-dB}$  is at 4.725 kHz and the low frequency gain is 20.8 dB. The magnitude and phase at 1 kHz is 7.04 dB and  $-101.9^\circ$  respectively.

Transient Plots:



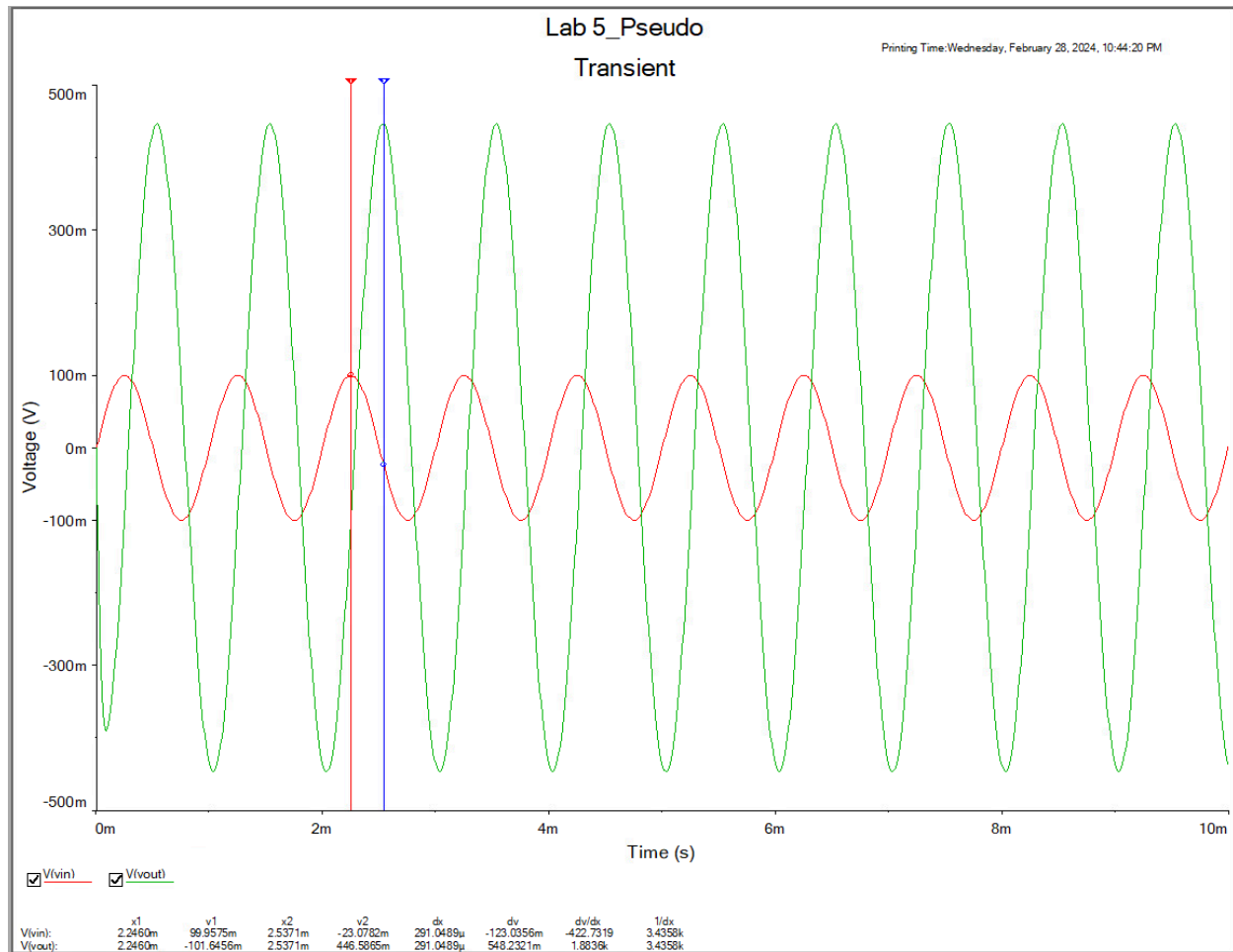

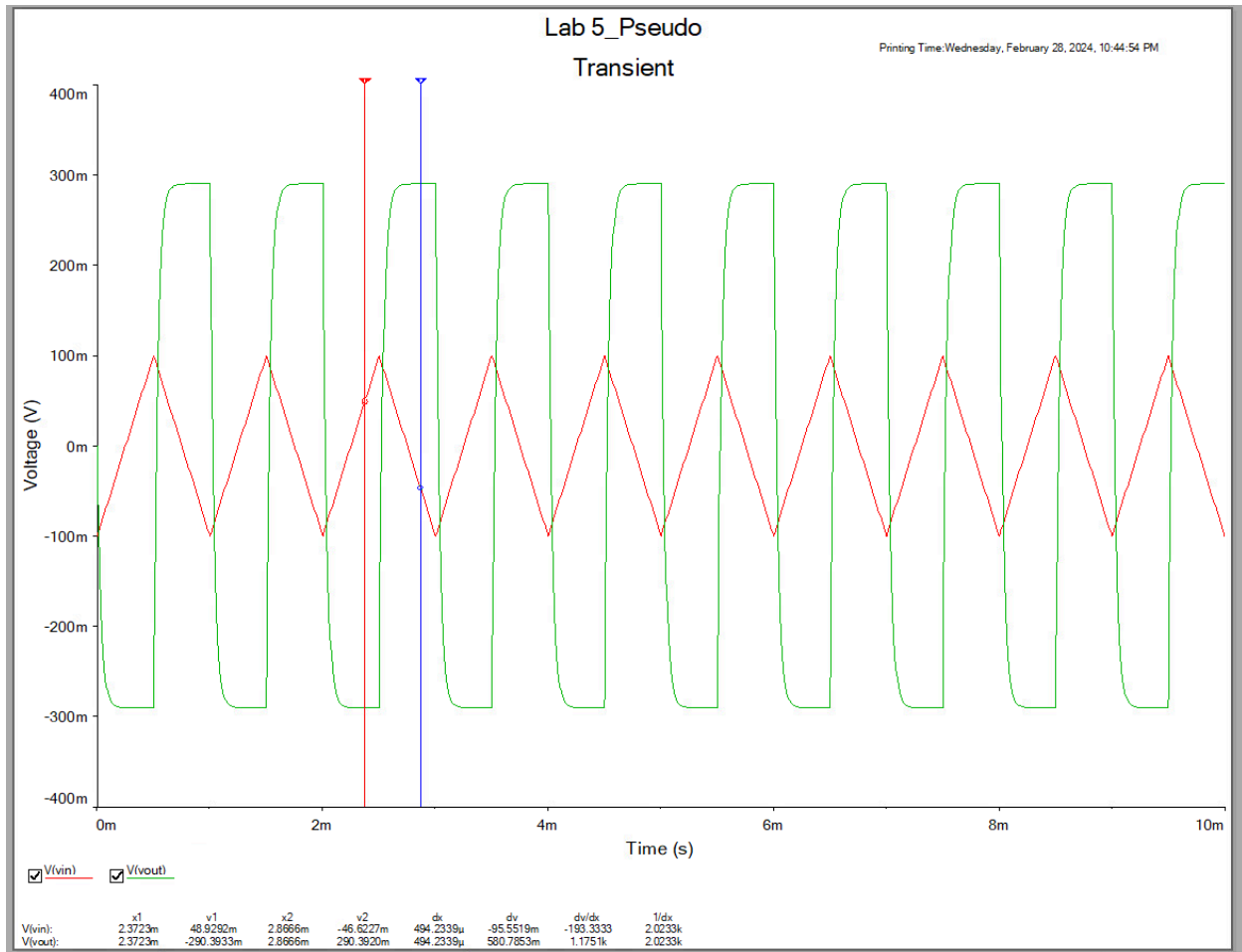The magnitudes of  $V_{in}$  and  $V_{out}$  are 0.0999 V and 0.4466 V respectively. The phase difference between the two waves is about  $98.9^\circ$  or 1.73 rad.




The  $V_{pp}$  for  $V_{in}$  and  $V_{out}$  is 0.2 V and 0.5808 V respectively.

### Finite GBW Limitations

Bode Plots:




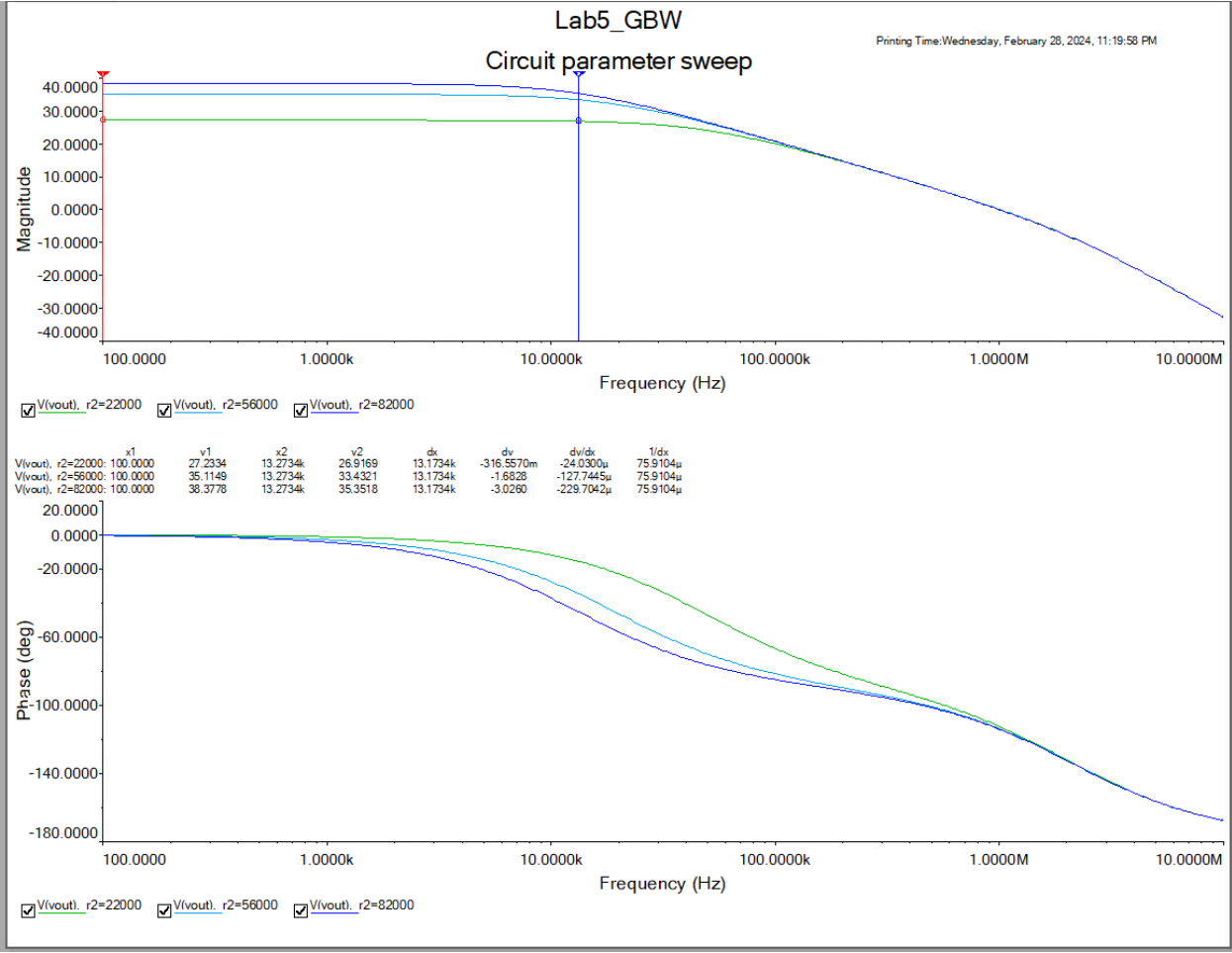

# Lab5\_GBW


Printing Time: Wednesday, February 28, 2024, 11:20:59 PM

## Circuit parameter sweep

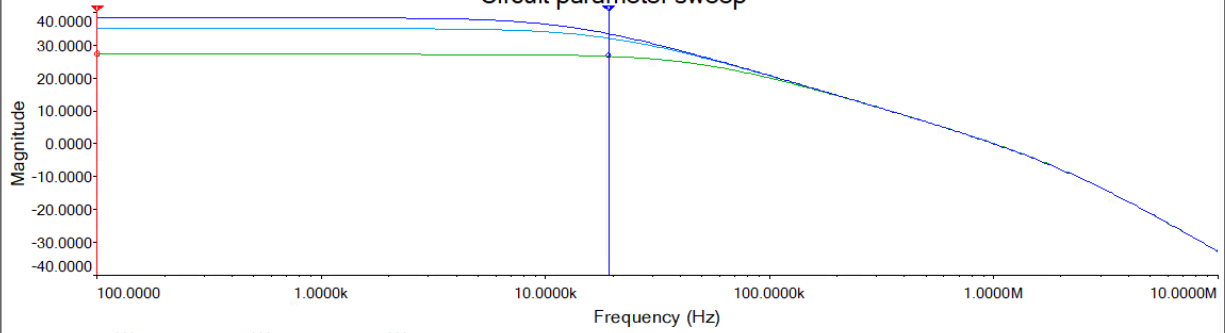


☒ V(vout), r2=22000 ☒ V(vout), r2=56000 ☒ V(vout), r2=82000

	x1	v1	x2	v2	dx	dv	dv/dx	1/dx
V(vout), r2=22000:	100.0000	27.2334	19.1241k	26.6003	19.0241k	-633.1736m	-33.2628u	52.5650u
V(vout), r2=56000:	100.0000	35.1149	19.1241k	32.1430	19.0241k	-2.9720	-156.2224u	52.5650u
V(vout), r2=82000:	100.0000	38.3778	19.1241k	33.4770	19.0241k	-4.9008	-257.6119u	52.5650u

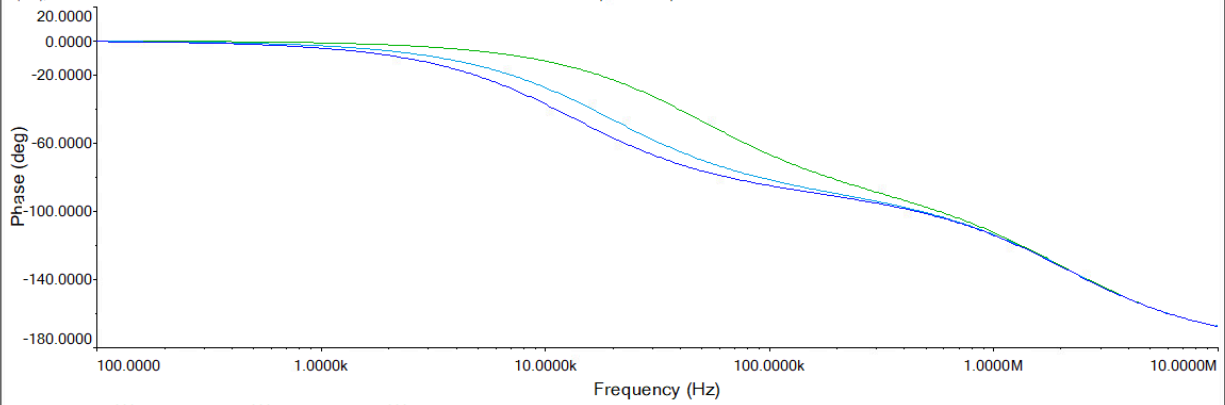

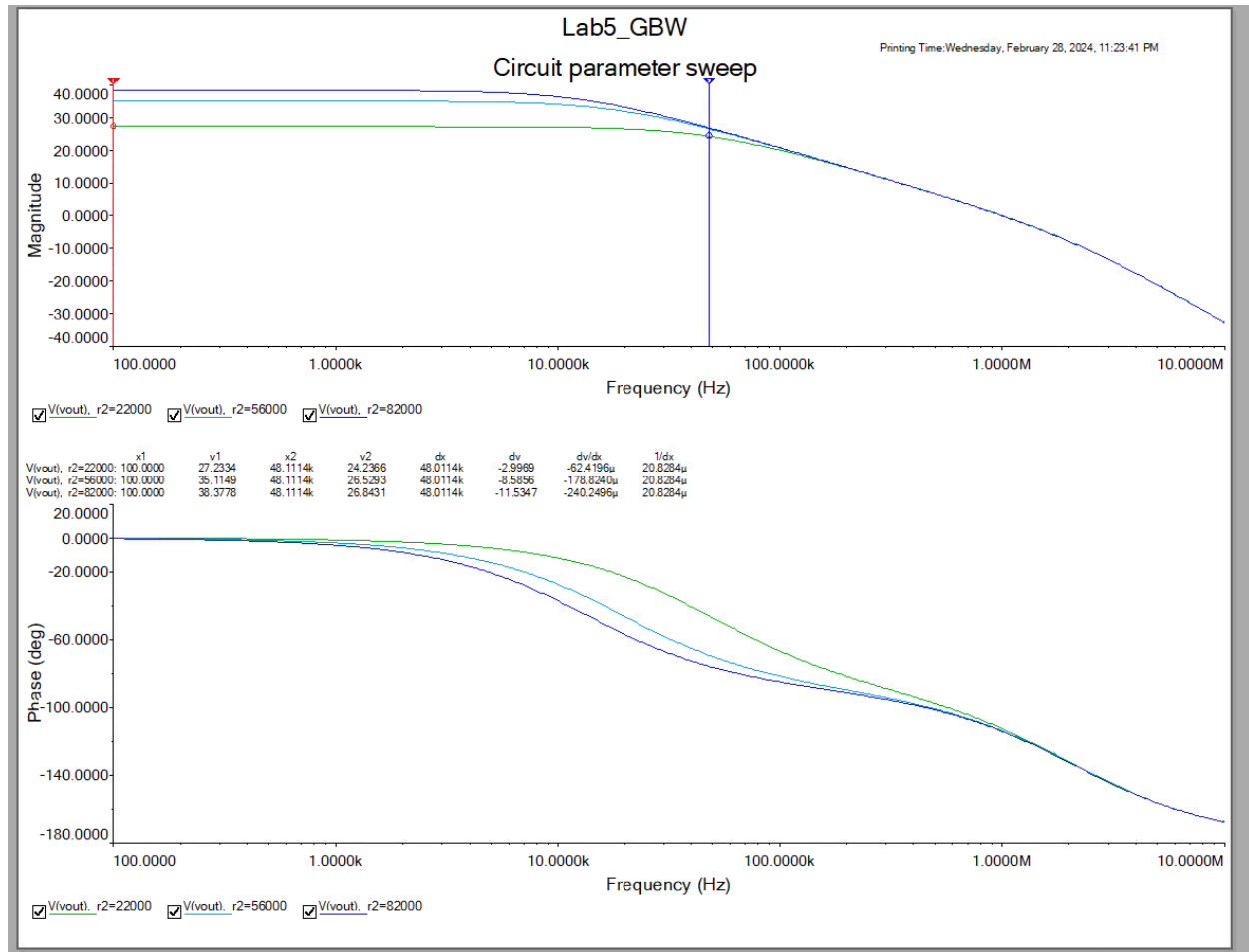☒ V(vout), r2=22000 ☒ V(vout), r2=56000 ☒ V(vout), r2=82000





The  $f_{3-dB}$  for R2 values 82k, 56k, and 22k are 13.273 kHz, 19.124 kHz, and 48.111 kHz respectively. The low frequency gain for R2 values 82k, 56k, and 22k are 27.23 dB, 35.11 dB, and 38.38 dB respectively.



## Slew Rate Limitations

Bode Plots:

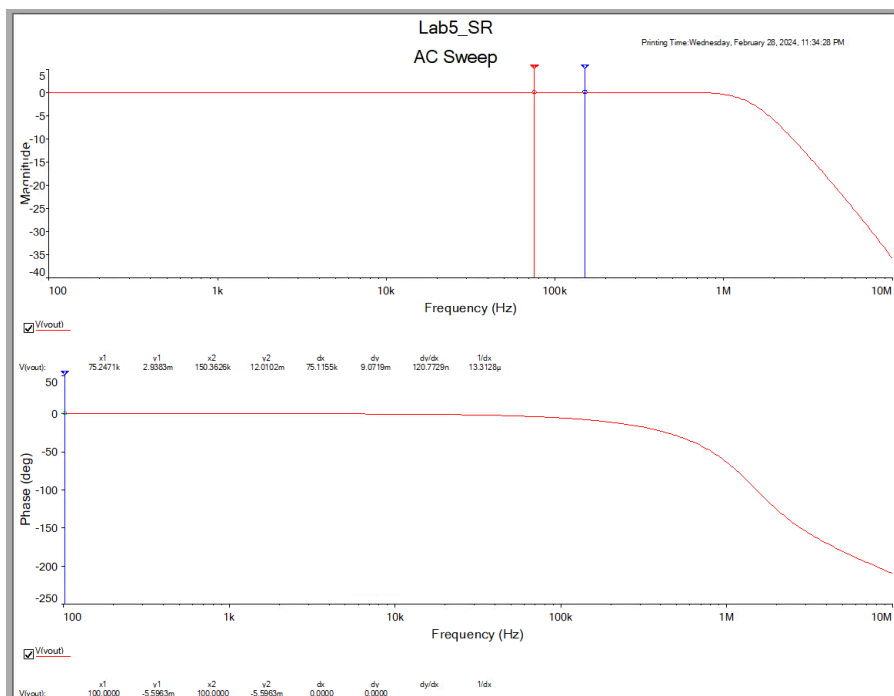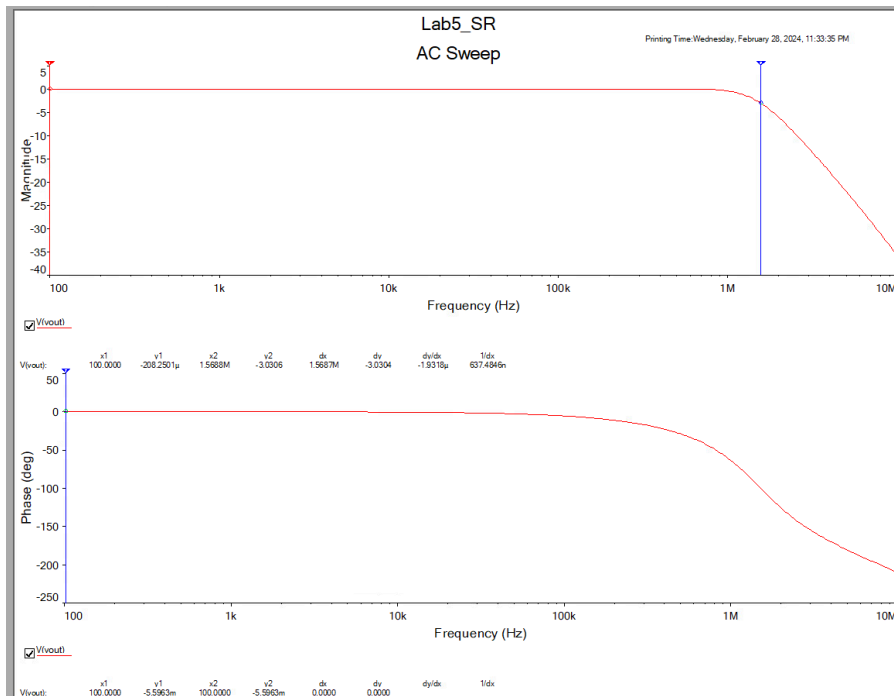


The low frequency gain is 0 dB and the  $f_{-3\text{dB}}$  is 1.57 MHz. The magnitude at 75 kHz and 150 kHz is 0.0029 dB and 0.012 dB respectively.

Transient Plots:

# Lab5\_SR

Printing Time: Wednesday, February 28, 2024, 11:37:53 PM

## Transient

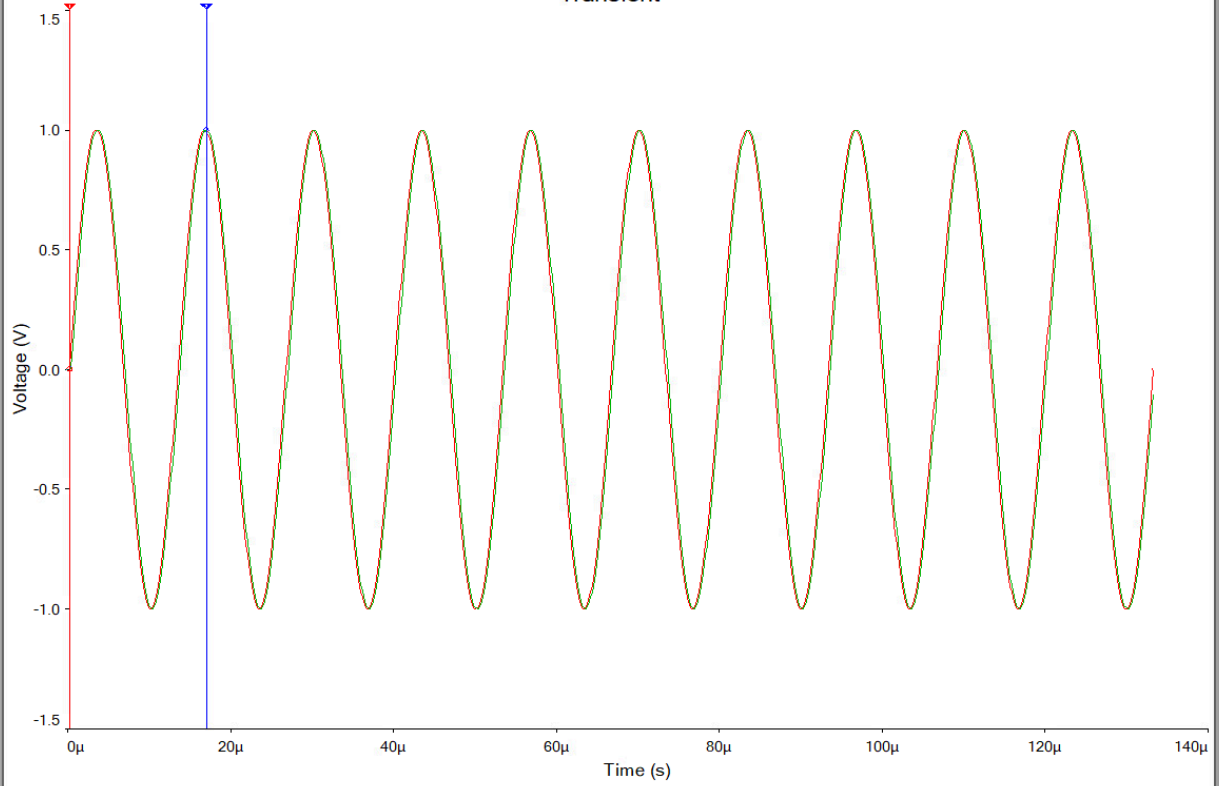


☒ V(vin) ☒ V(vout)

V(vin):	x1	v1	x2	v2	dx	dv	dv/dx	1/dx
V(vout):	0.0000	0.0000	16.8152 $\mu$	997.5026m	16.8152 $\mu$	997.5026m	59.3214k	59.4699k
	0.0000	11.1842 $\mu$	16.8152 $\mu$	1.0003	16.8152 $\mu$	1.0003	59.4877k	59.4699k

# Lab5\_SR


Printing Time: Wednesday, February 28, 2024, 11:41:58 PM

## Transient

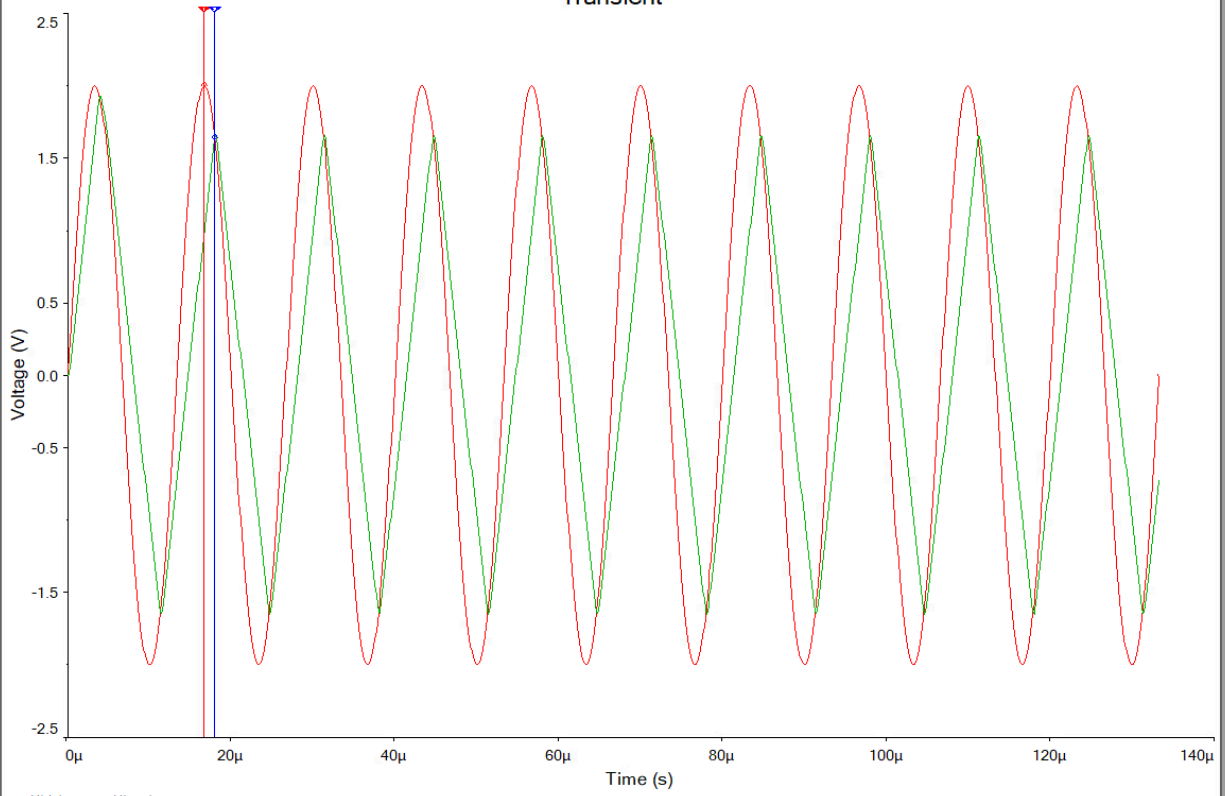

	x1	v1	x2	v2	dx	dv	dv/dx	1/dx
V(vin):	16.6630μ	1.9991	17.9565μ	1.6411	1.2935μ	-358.0258m	-276.7931k	773.1092k
V(vout):	16.6630μ	994.7117m	17.9565μ	1.6397	1.2935μ	644.9429m	496.6113k	773.1092k



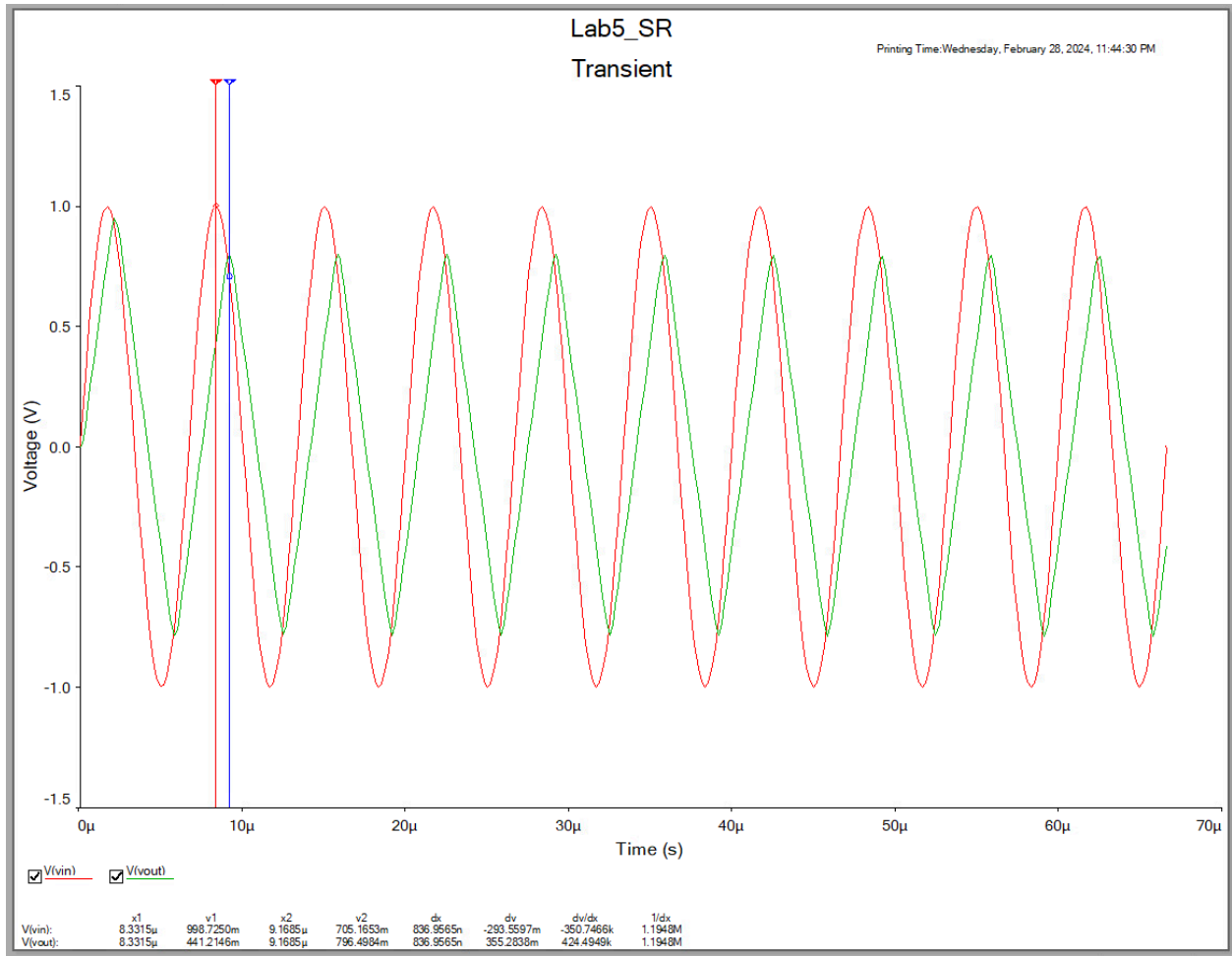

Fourier Plots:

## Lab5\_SR

Printing Time: Wednesday, February 28, 2024, 11:40:43 PM

1	Fourier analysis for V(vout				
2	DC component:	9.13295e-06			
3	No. Harmonics:	9			
4	THD:	0.939528 %			
5	Grid size:	256			
6	Interpolation Degree:	1			
7					
8	Harmonic	Frequency	Magnitude	Phase	Norm. Mag
9	0	0	9.13295e-06	0	9.14567e-06
10	1	75000	0.998609	-5.3684	1
11	2	150000	0.000235828	-19.427	0.000236157
12	3	225000	0.00913983	-123.91	0.00915256
13	4	300000	9.02378e-05	-60.166	9.03635e-05
14	5	375000	0.00202855	-174.91	0.00203137
15	6	450000	3.27862e-05	-121.8	3.28318e-05
16	7	525000	0.00053193	114.627	0.000532671
17	8	600000	1.24114e-05	160.194	1.24287e-05
18	9	675000	0.000162323	31.5573	0.000162549
19					

The THD at 1 V, 75 kHz is 0.9395%

# Lab5\_SR

Printing Time: Wednesday, February 28, 2024, 11:42:47 PM

1	Fourier analysis for V(vout)				
2	DC component:	0.00118459			
3	No. Harmonics:	9			
4	THD:	11.793 %			
5	Grid size:	256			
6	Interpolation Degree:	1			
7					
8	Harmonic	Frequency	Magnitude	Phase	Norm. Mag
9	0	0	0.00118459	0	0.000857177
10	1	75000	1.38197	-37.382	1
11	2	150000	0.00416772	-126.98	0.00301578
12	3	225000	0.151119	68.0055	0.10935
13	4	300000	0.00122769	-3.9273	0.000888362
14	5	375000	0.0529583	173.496	0.0383209
15	6	450000	0.000695514	112.471	0.000503277
16	7	525000	0.0259969	-80.715	0.0188115
17	8	600000	0.000478892	-135.09	0.000346528
18	9	675000	0.0149815	25.4241	0.0108407
19					

The THD at 2 V, 75 kHz is 11.793%



## Lab5\_SR

Printing Time: Wednesday, February 28, 2024, 11:46:24 PM

1	Fourier analysis for V(vout)				
2	DC component:	2.84679e-05			
3	No. Harmonics:	9			
4	THD:	11.326 %			
5	Grid size:	256			
6	Interpolation Degree:	1			
7					
8	Harmonic	Frequency	Magnitude	Phase	Norm. Mag
9	0	0	2.84679e-05	0	4.1402e-05
10	1	150000	0.687597	-42.563	1
11	2	300000	0.00104431	-134.44	0.00151878
12	3	450000	0.0729918	52.6309	0.106155
13	4	600000	0.000303939	-20.92	0.00044203
14	5	750000	0.0241447	148.573	0.0351146
15	6	900000	0.000164118	86.026	0.000238684
16	7	1.05e+06	0.0109508	-114.37	0.0159262
17	8	1.2e+06	0.00010481	-170.31	0.000152429
18	9	1.35e+06	0.00574031	-16.107	0.00834836
19					

The THD at 150 kHz is 11.326%